

Short Ques
Logical Ques

CSE-2103

Computer Architecture



Lecture – 1, 2

Text Books

- ***Computer Architecture and Organization***
Hayes J.P., McGraw-Hill.
- ***Computer organization and design: The hardware/software interface***
Patterson D.A., Hennessy J.L., Morgan Kaufmann.



Reference Book


- ***Computer Architecture: A Quantitative Approach***
Patterson D.A., Hennessy J.L., Morgan Kaufmann.



Fixed-Point Arithmetic

- Addition
- Subtraction
- Multiplication
- Division

Half Adder

 


$X_0 Y_0$	$S_0 C_0$
0 0	0 0
0 1	1 0
1 0	1 0
1 1	1 1

$$S_0 = X_0 \oplus Y_0$$

$$C_0 = X_0 Y_0$$

Full Adder


 


Inputs			Outputs	
x_0	y_0	c_{-1}	c_0	s_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S_0 = X_0 \oplus Y_0 \oplus C_{-1}$$

$$C_0 = X_0 Y_0 + X_0 C_{-1} + Y_0 C_{-1}$$

Full Adder

 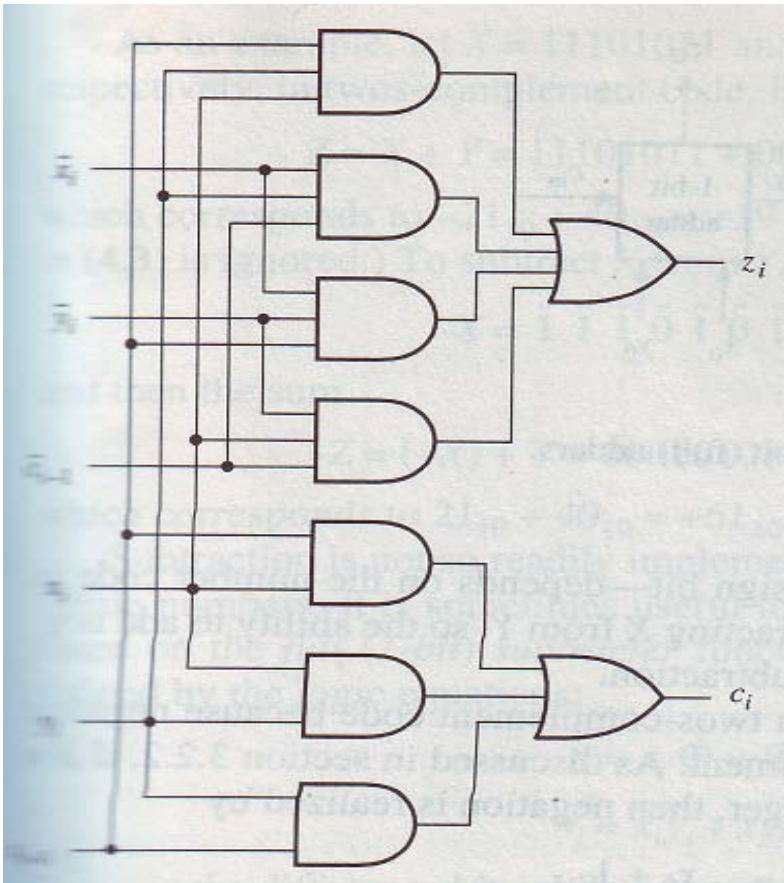


Serial Binary Adder

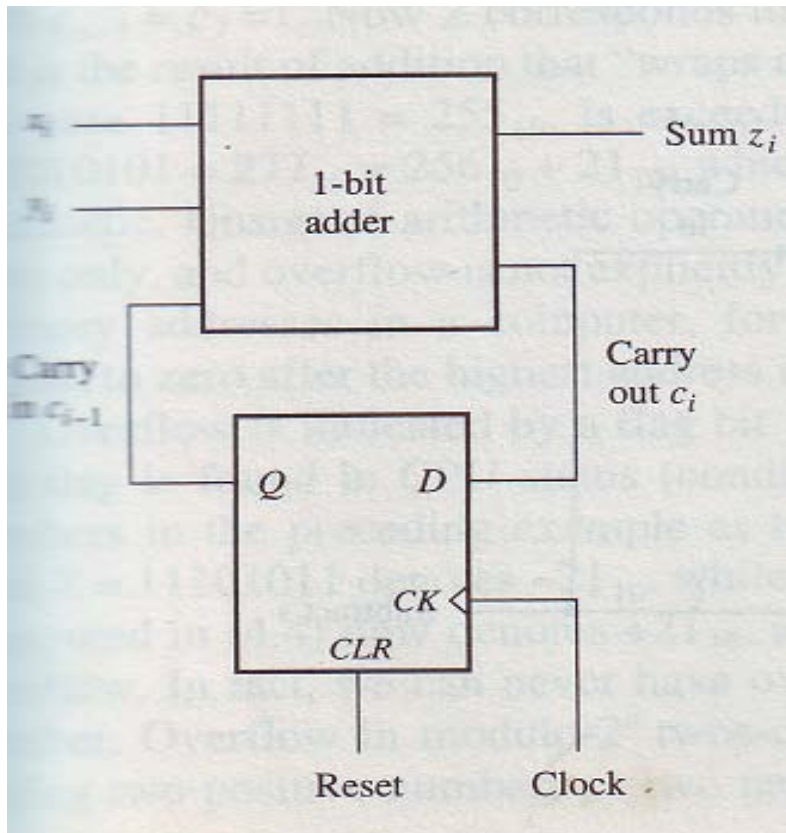


- Least expensive circuit in terms of hardware cost.
- It adds the numbers bit by bit and so requires n clock cycle to compute the sum of two n -bit numbers.
- Circuit size independent of n .

Ripple Carry Adder

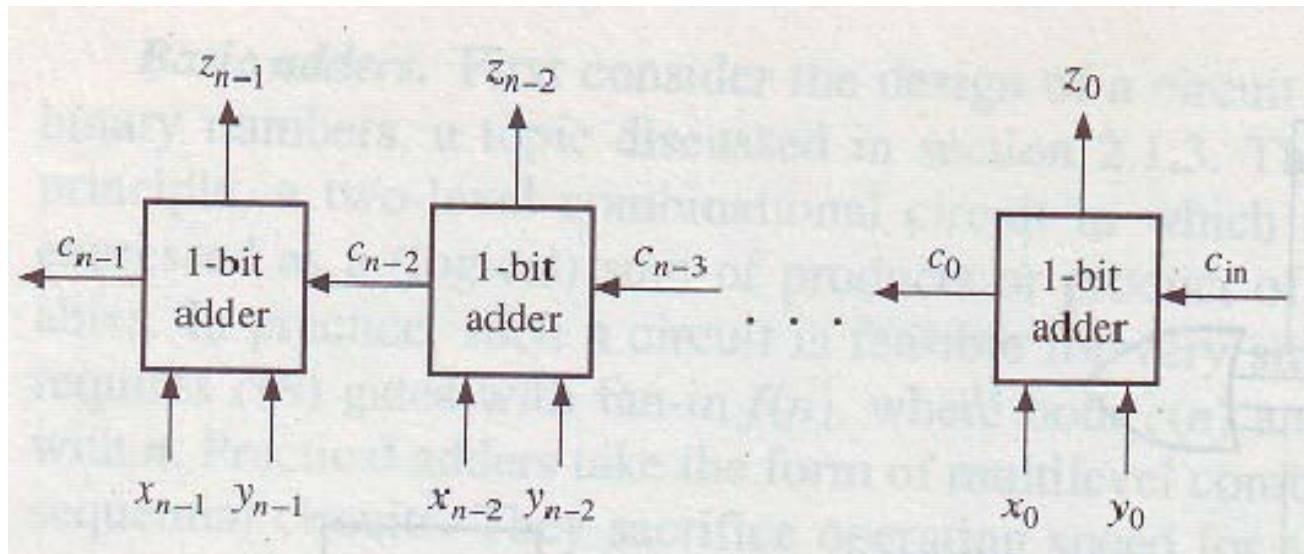

- A 1 appearing on the carry in line of a 1-bit adder causes it to generate a 1 on its carry out line. So, the carry signal propagates through the adder from right to left.
- The maximum signal propagation delay is nd , where d is the delay of a full-adder stage.
- The amount of hardware increases linearly with n .


2's Complement Adder-Subtractor

 

- When $s = 0$, then $X \oplus s = X$
- When $s = 1$, then $X \oplus s = \bar{X}$

2's Complement Adder-Subtractor

Example: Adder/Subtractor

 

Overflow

- When the result of an arithmetic operation exceeds the standard word size n , overflow occurs.
- Example: let $n=8$, $X=11101011=235_{10}$ and $Y=00101010=42_{10}$
 $Z = X+Y = 11101011 + 0101010 = 00010101 = 21_{10}$
with $C_{n-1} = C_7 = 1$.
 $C_7Z = 100010101 = 277_{10} = 256_{10} + 21_{10}$
- The result of an addition simply wraps around when the largest number 2^n-1 is exceeded.
- For n , the number range for unsigned number is 0 to 2^n-1

Overflow

- We can never have overflow on adding a negative and positive number.
- Example: let $n=8$ $X=11101011=-21_{10}$ and $Y=00101010=+42_{10}$
 $Z = X+Y = 00010101 = 21_{10}$ and $C_7 = 1$.
So, $C_{n-1} = 1$ does not indicate overflow.
- Overflow in 2's complement addition can result from adding
 - 1) two positive numbers or
 - 2) two negative numbers.

Overflow

Case 1: Two numbers are positive.

Let $n = 4$, $7 + 3 = 0111 + 0011 = 1010$ so, $c_{n-2} = 1$

$C_{n-2} = 1$ indicates that the magnitude of the sum exceeds the $n-1$ bits allocated to it.

Case 2: Two numbers are negative.

Let $n=4$, $-7 = 1001$, $-3 = 1101$

so, $1001 + 1101 = 10110$ so, $c_{n-2} = 0$

$C_{n-2} = 0$ indicates the overflow.

Overflow

$$Z_{n-1}Z_{n-2}\dots Z_0 := X_{n-1}X_{n-2}\dots X_0 + Y_{n-1}Y_{n-2}\dots Y_0$$

$$V = \overline{X_{n-1}}\overline{Y_{n-1}}C_{n-2} + X_{n-1}Y_{n-1}\overline{C_{n-2}}$$

$$V = C_{n-1} \oplus C_{n-2}$$

Overflow Rules Table

Number Type	Overflow Detection	When It Happens
Unsigned	$C_n = 1$	Sum > $2^n - 1$
Signed (2's complement)	$C_n \oplus C_{n-1} = 1$	Positive + Positive = Negative, Negative + Negative = Positive

X_{n-1}	Y_{n-1}	C_{n-2}	Z_{n-1}	v
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0




Carry-Lookahead Adder

- It reduce the time required to form carry signals.
- It computes the input carry needed by stage i directly from carrylike signals obtained from all the preceding stages $i-1$, $i-2$,, 0 , rather than waiting for normal carries to ripple slowly from stage to stage.
- Adders that use this principle are called carry-lookahead adders.

Carry-Lookahead Adder

 
- Two signals:
generate signal, $g_i = x_i y_i$
propagate signal, $p_i = x_i + y_i$
- $c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$
- $c_i = g_i + p_i c_{i-1}$
- $c_{i-1} = g_{i-1} + p_{i-1} c_{i-2}$
- $c_i = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-2}$



4-bit Carry-Lookahead Adder

- $c_i = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-2}$
- $c_0 = g_0 + p_0 c_{in}$
 $c_1 = g_1 + p_1 g_0 + p_1 p_0 c_{in}$
 $c_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_{in}$
 $c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_{in}$
- $z_i = x_i \oplus y_i \oplus c_{i-1}$ can be written as $z_i = p_i \oplus g_i \oplus c_{i-1}$

4-bit Carry-Lookahead Adder

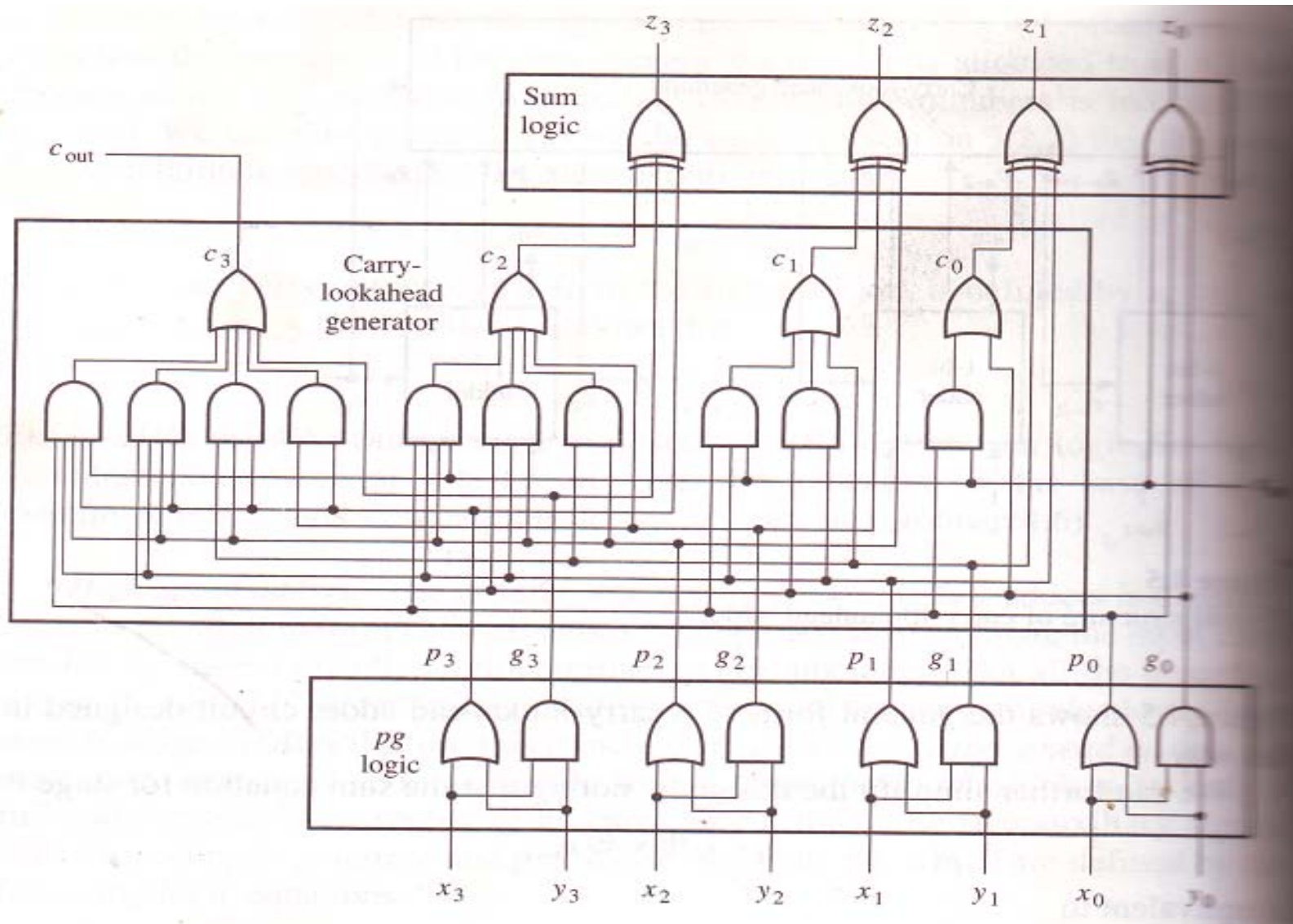


4-bit Carry-Lookahead Adder

- Maximum delay is $4d$, where d is the average gate delay. It is independent of number of input n .
- The number of gates grows in proportion to n^2 as n increases.
- The complexity of the carry generation logic in the carry lookahead adder, including its gate count, its maximum fan-in, and its maximum fan-out, increase steadily with n .
- It limits n to 4.

Adder Expansion

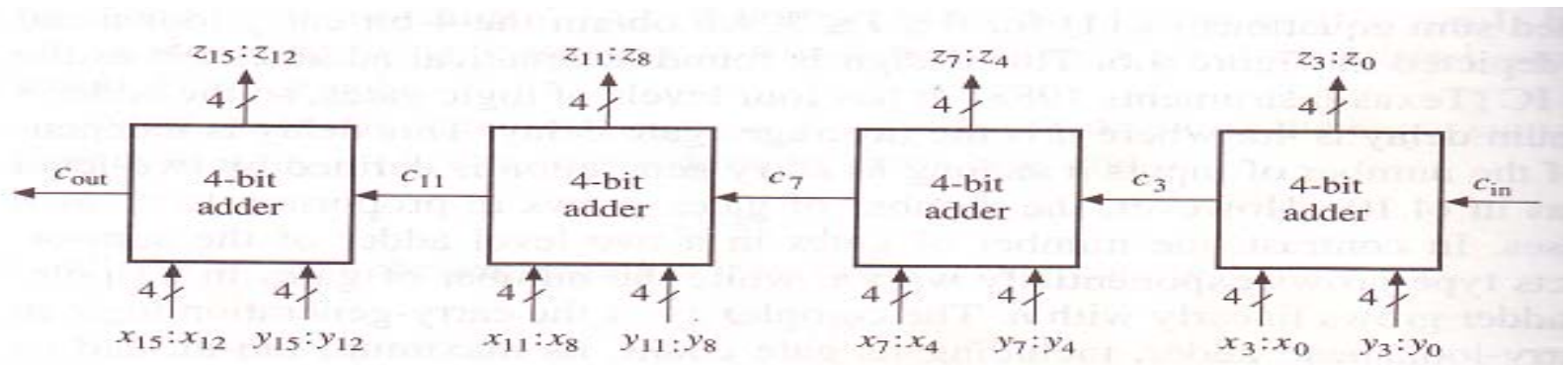
- If we replace n 1-bit adder stages in the n -bit ripple carry adder with n k -bit adders, we obtain an nk -bit adder.



16-bit adder composed of 4-bit adders linked by ripple-carry propagation

Adder Expansion

 - If we replace n 1-bit adder stages in the n -bit carry look-ahead adder with n k -bit adders, we obtain an nk -bit adder.




16-bit adder composed of 4-bit adders linked by carry look-ahead

$$g = x_i y_i + x_{i-1} y_{i-1} (x_i + y_i) + x_{i-2} y_{i-2} (x_i + y_i) (x_{i-1} + y_{i-1})$$


$$+ x_{i-3} y_{i-3} (x_i + y_i) (x_{i-1} + y_{i-1}) (x_{i-2} + y_{i-2})$$

$$p = (x_i + y_i) (x_{i-1} + y_{i-1}) (x_{i-2} + y_{i-2}) (x_{i-3} + y_{i-3})$$


Complete 2's Complement Adder-Subtractor

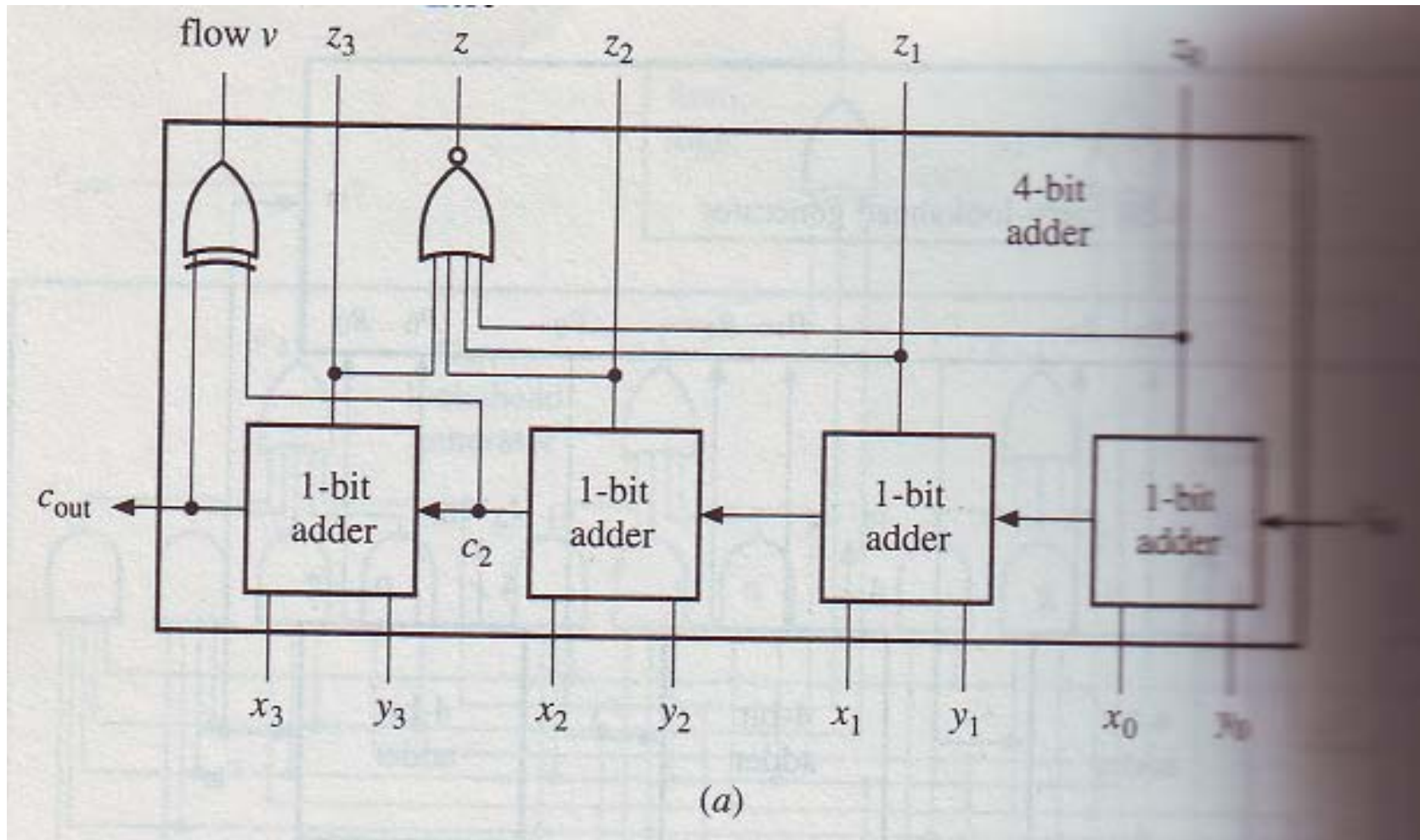

Complete 2's Complement Adder-Subtractor

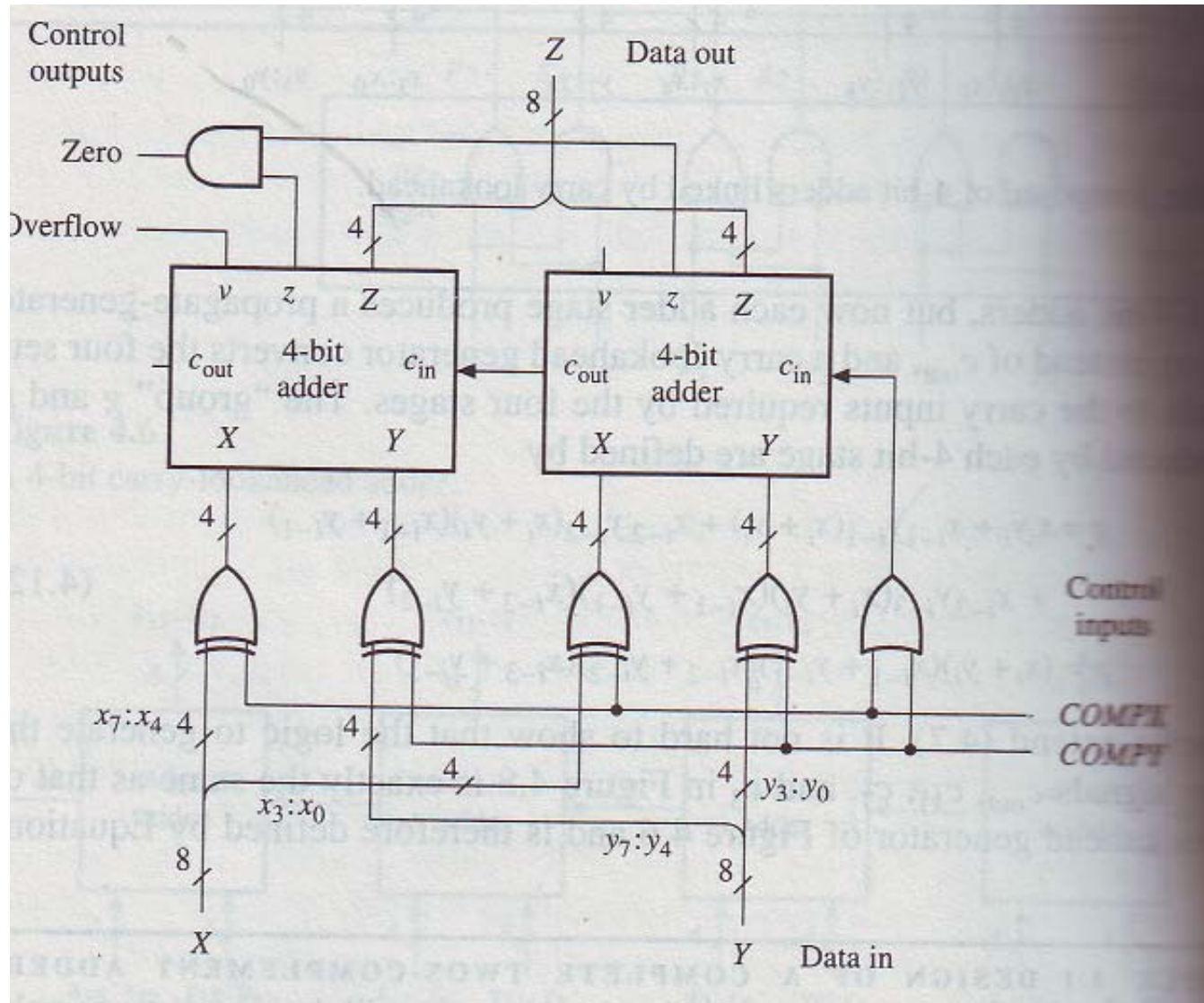

Carry-Save Adder

 

Carry-Save Adder

- One of the major speed enhancement techniques used in modern digital circuits is the ability to add numbers with minimal carry propagation.
- The basic idea is that three numbers can be reduced to 2, in a 3:2 compressor, by doing the addition while keeping the carries and the sum separate.

10111001
 00101010
00111001
 Sum: 10101010
 Carry: 00111001
 Result: 100011100

no prop delay
no prop delay
only 1 Propagation delay

A
 + B
 + C
 + D
 + E

no 9 prop delay
only 1 prop delay

$S =$
 $C =$

- The sum and carry can then be recombined in a normal addition to form the correct result.