 


# Lecture 21:



# Building a Datapath

CMPS 221 – Computer Organization and Design

# Part 3: Microarchitecture



# Microarchitecture

  

```

sll $2, $1, 5
add $2, $2, $1
lw  $16, 0($2)
sw  $16, 0($2)
$w  $15, 4($2)
jr  $31, $2
    
```


# Introduction

- CPU performance factors
  - Instruction count
    - Determined by ISA and compiler
  - CPI and Cycle time
    - Determined by CPU hardware
- We will examine two MIPS implementations
  - A simple version
  - A more realistic pipelined version
- Focus on a simple subset (shows most aspects)
  - Arithmetic/logical: add, addi
  - Memory reference: lw, sw
  - Control transfer: beq, j

# Building a Datapath


- A **datapath** is a set of elements that process data and addresses in the CPU
- Components of a MIPS datapath:
  - PC register, instruction memory (fetch instructions)
  - Register file (read/write registers)
  - ALUs:
    - Arithmetic/logic operations
    - Memory address for load/store
    - Branch target address
  - Data memory (load/store data)

# Instruction Fetch

 


PC register points to  
the current instruction  
to be executed

# Instruction Fetch

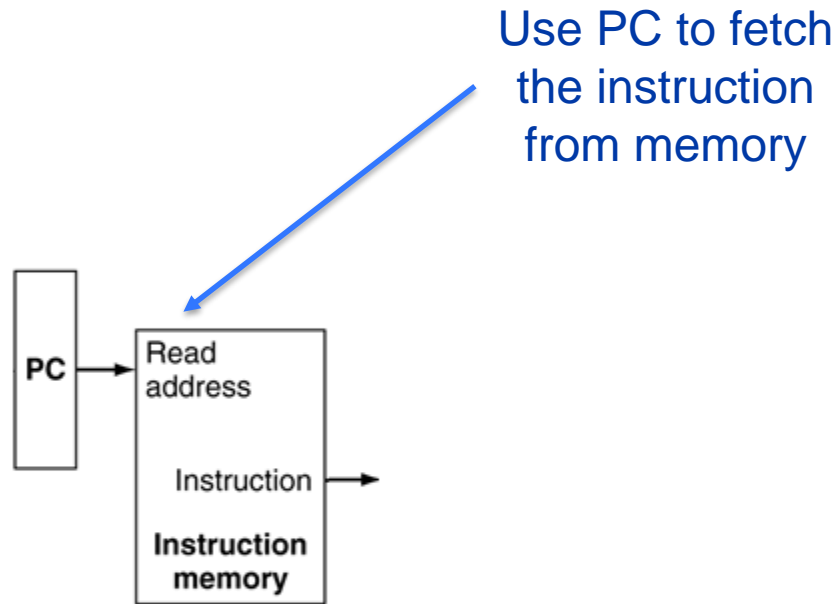


# Instruction Fetch

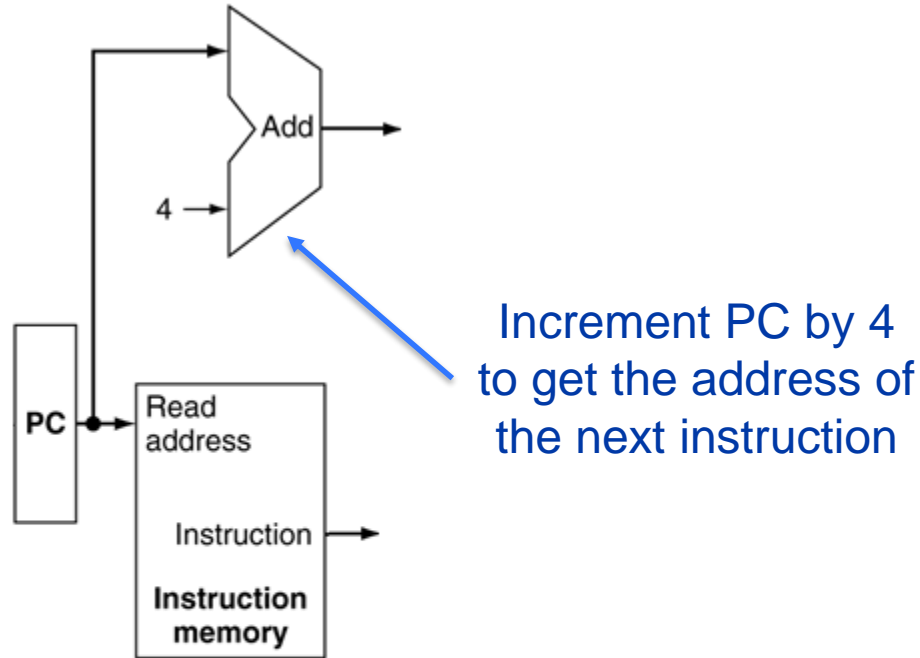




# Instruction Fetch

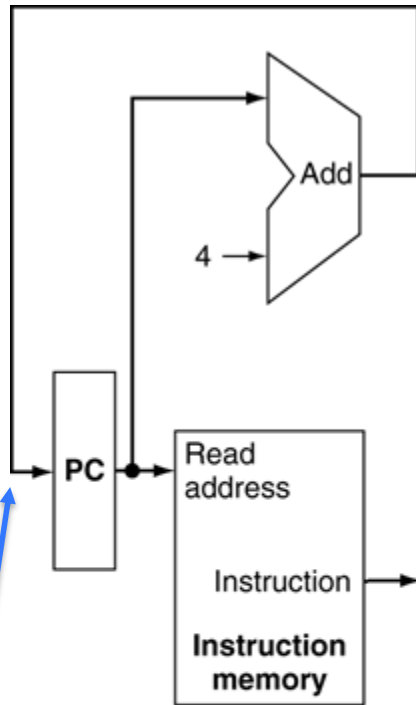

Update the PC register at the end of the cycle to fetch the next instruction on the next cycle


# R-type Instructions

add \$t1, \$a0, \$s2

 

# R-type Instructions

add \$t1, \$a0, \$s2

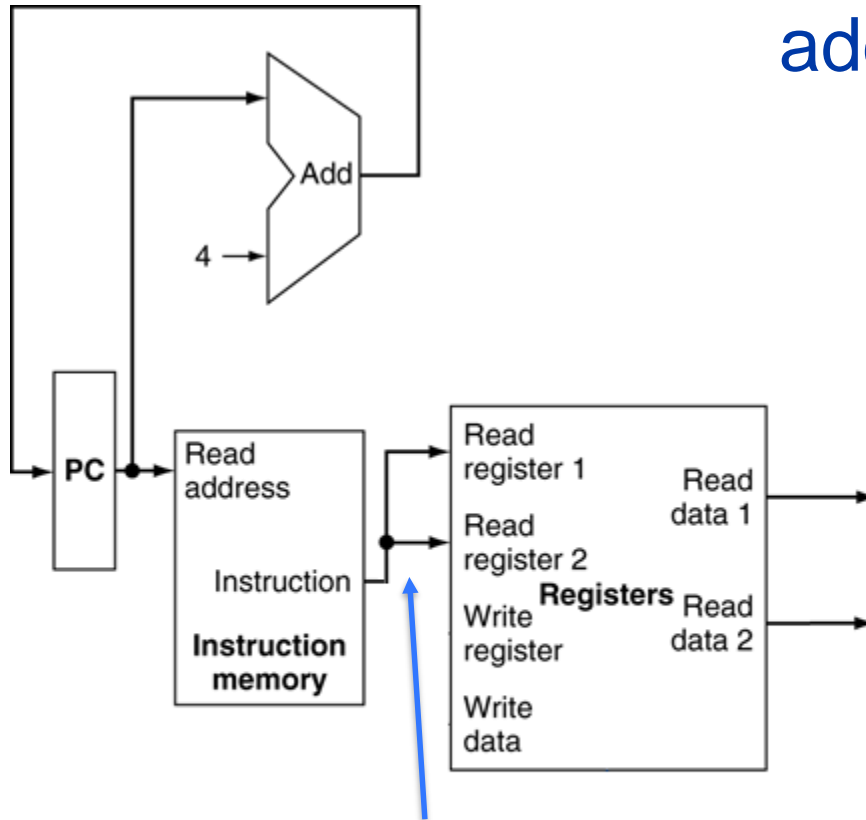


Use the source register numbers to read the source registers from the register file
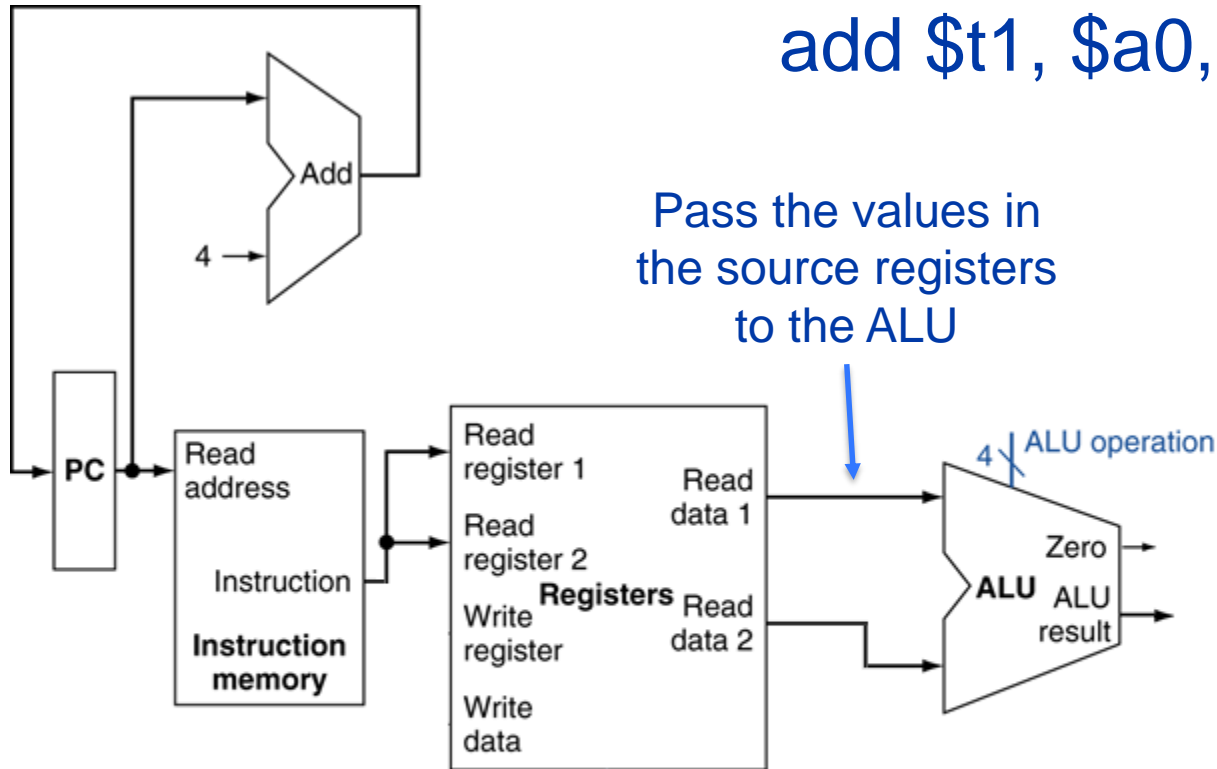
# R-type Instructions


add \$t1, \$a0, \$s2

Pass the values in  
the source registers  
to the ALU



# R-type Instructions


add \$t1, \$a0, \$s2

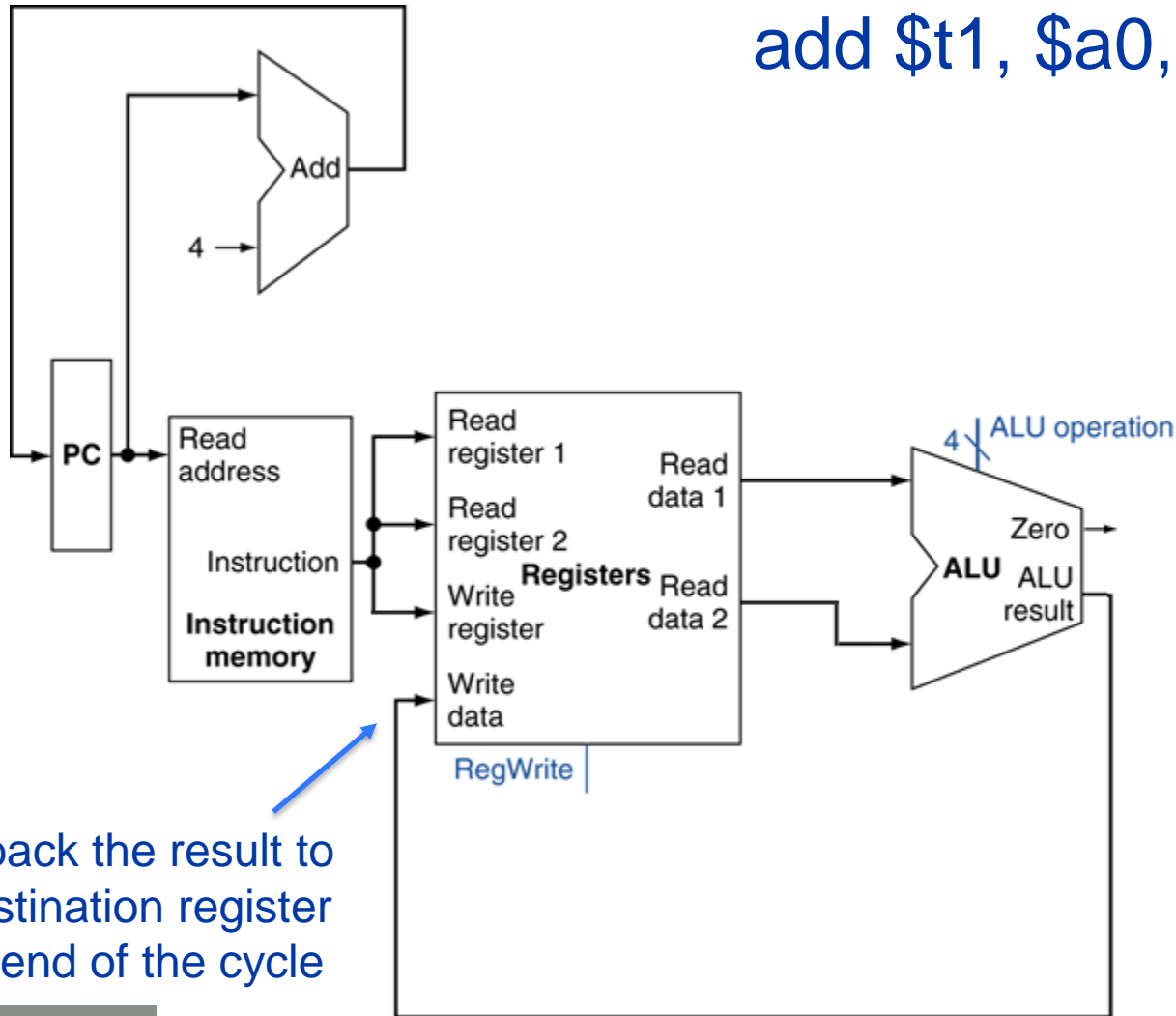

Write back the result to the destination register at the end of the cycle

# Immediate Instructions


`addi $t0, $s0, 4`

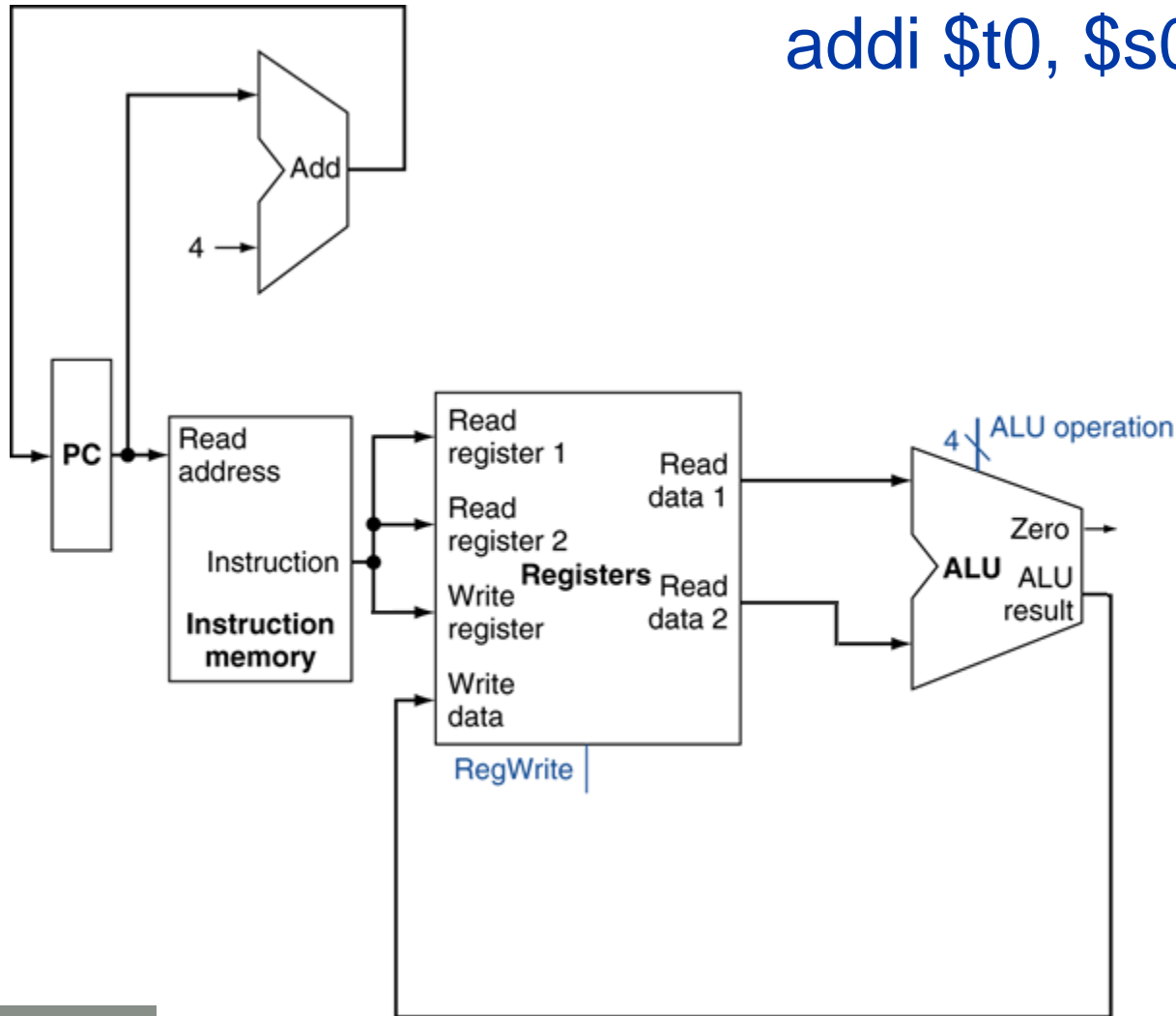
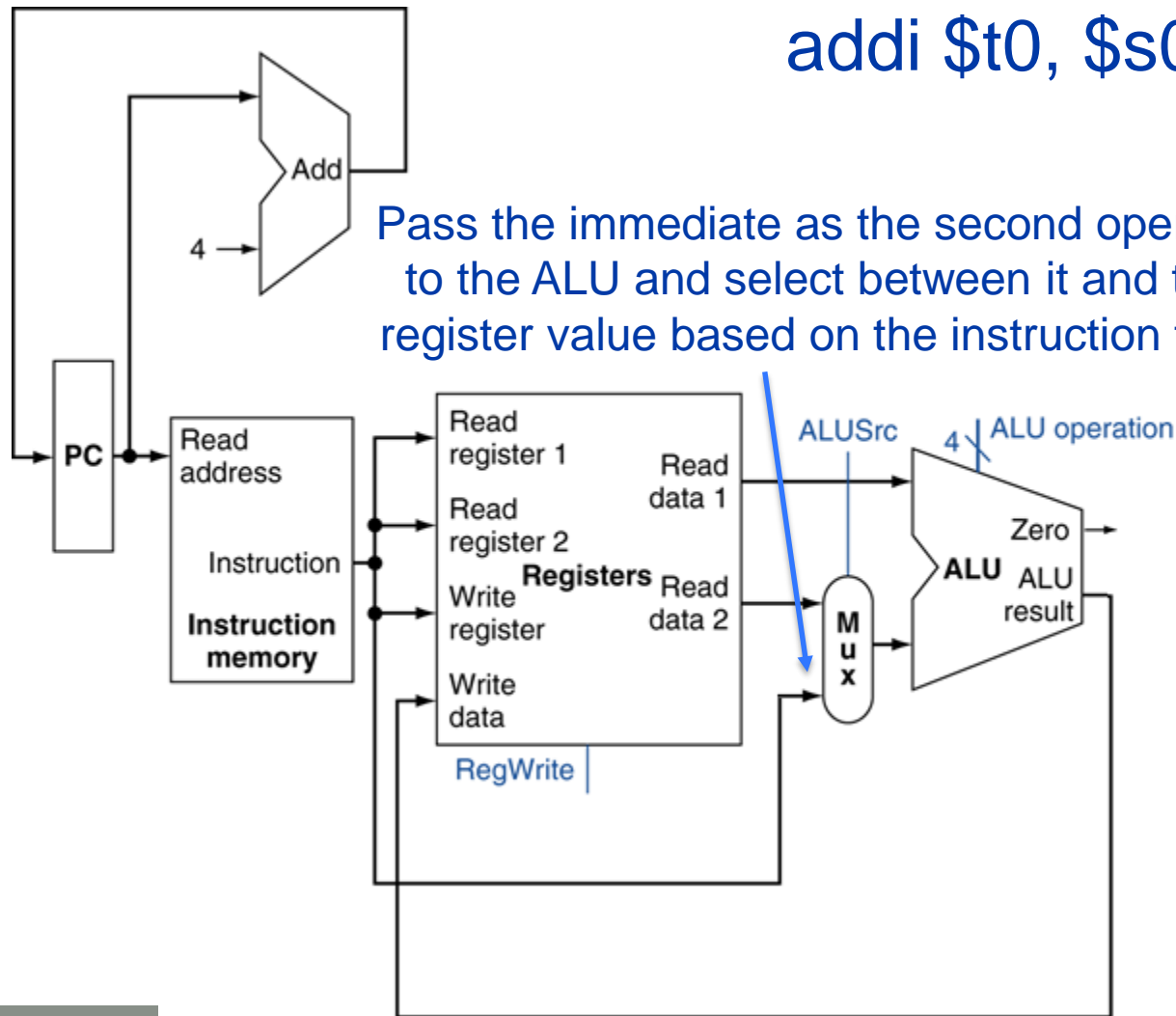
# Immediate Instructions


`addi $t0, $s0, 4`

Pass the immediate as the second operand to the ALU and select between it and the register value based on the instruction type



# Immediate Instructions


`addi $t0, $s0, 4`

 



# Load Instructions


`lw $s0, 8($t0)`

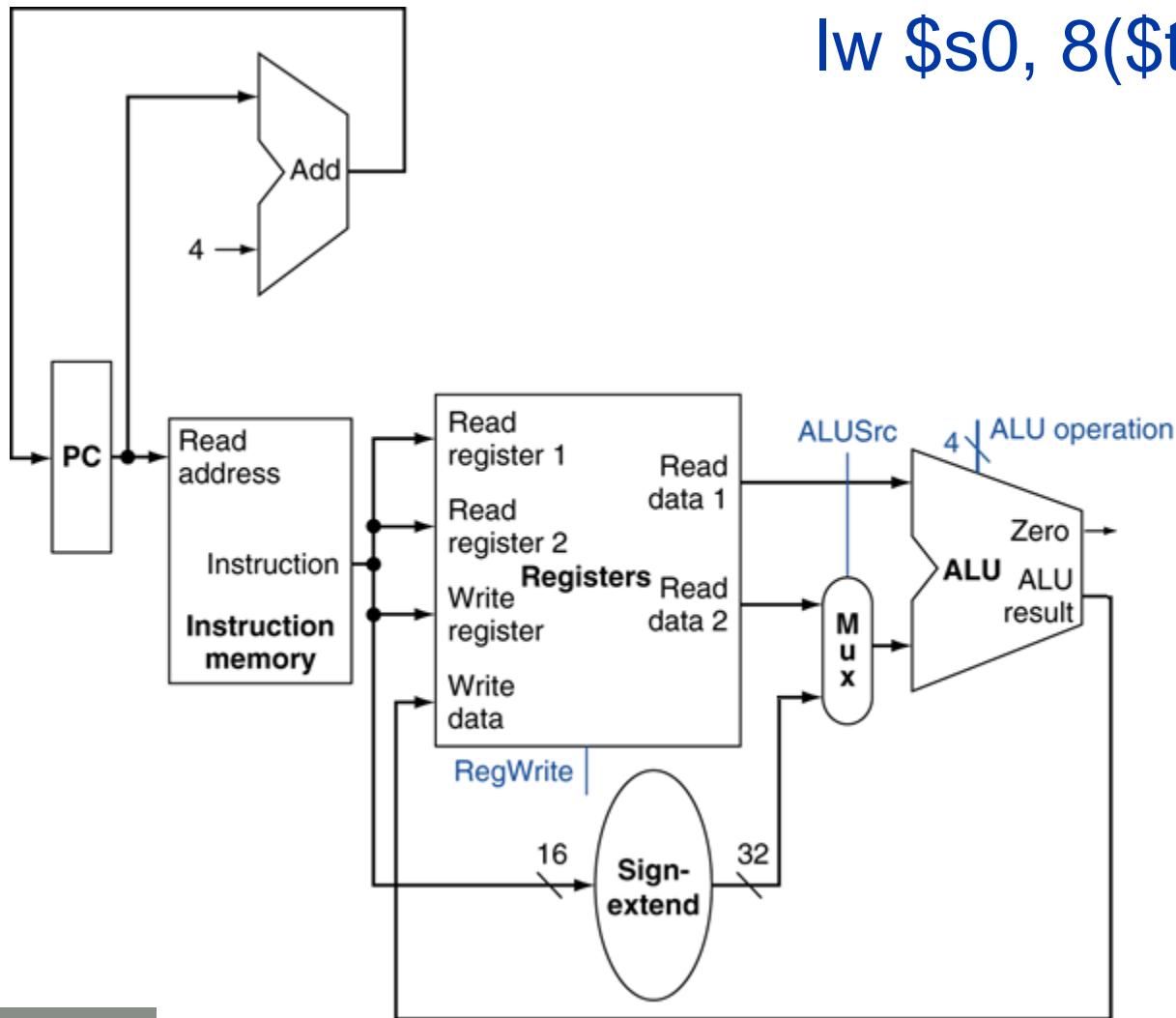
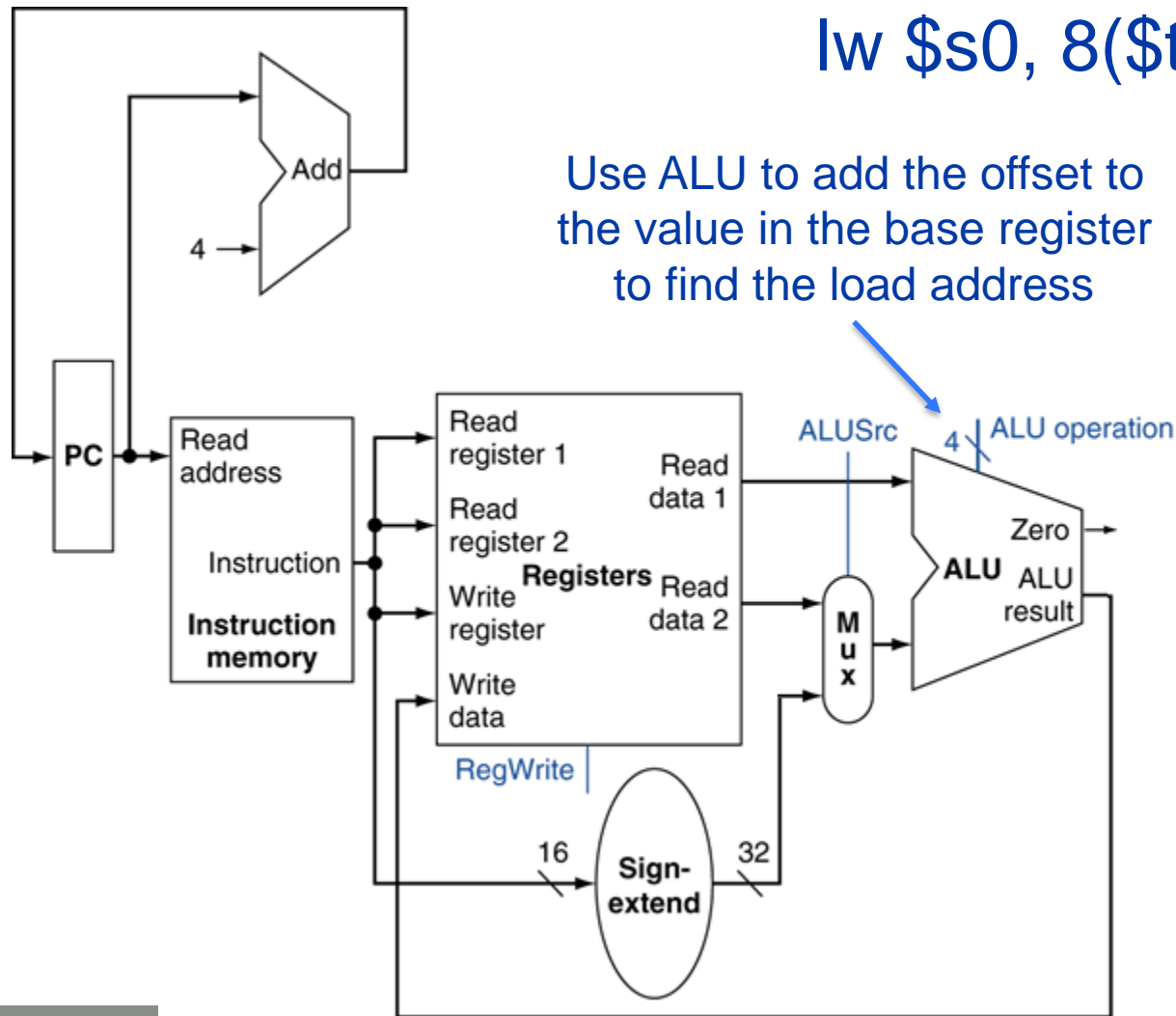
# Load Instructions

`lw $s0, 8($t0)`


Use ALU to add the offset to the value in the base register to find the load address


 
# Load Instructions

`lw $s0, 8($t0)`


Pass the load address  
to a data memory to  
load the value


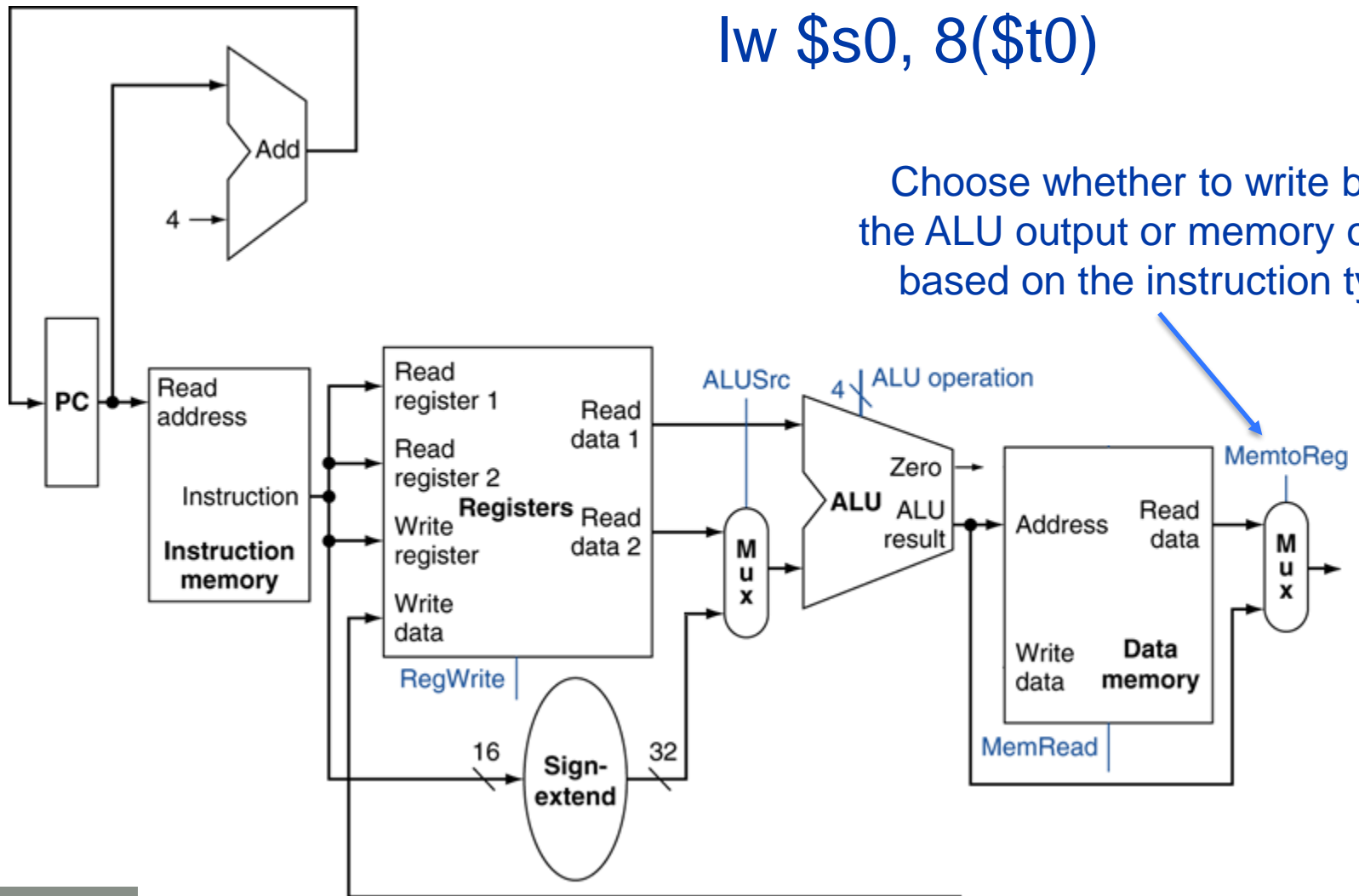
# Load Instructions


`lw $s0, 8($t0)`

Choose whether to write back  
the ALU output or memory output  
based on the instruction type




# Load Instructions

`lw $s0, 8($t0)`

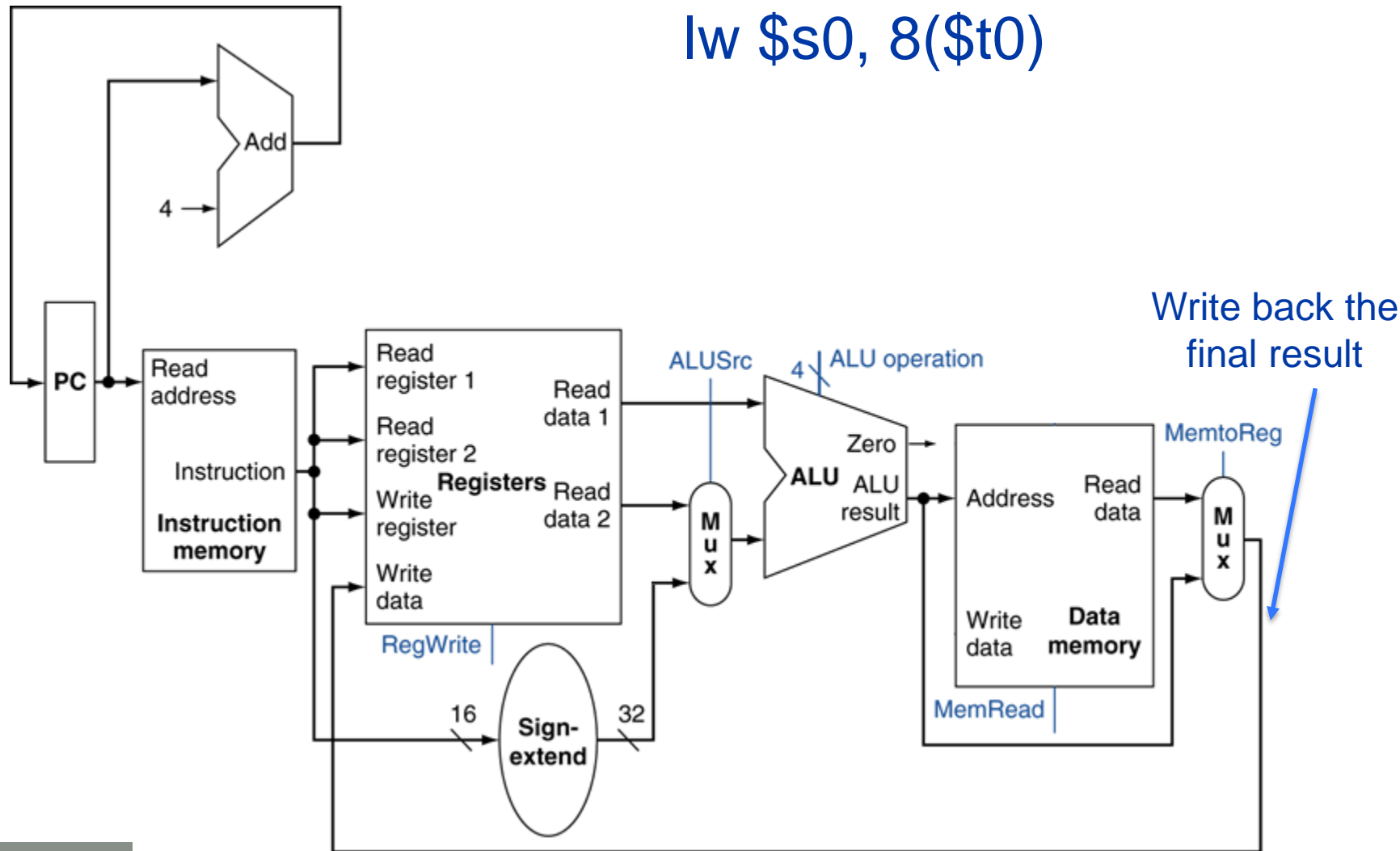

# Store Instructions


sw \$a0, 8(\$sp)

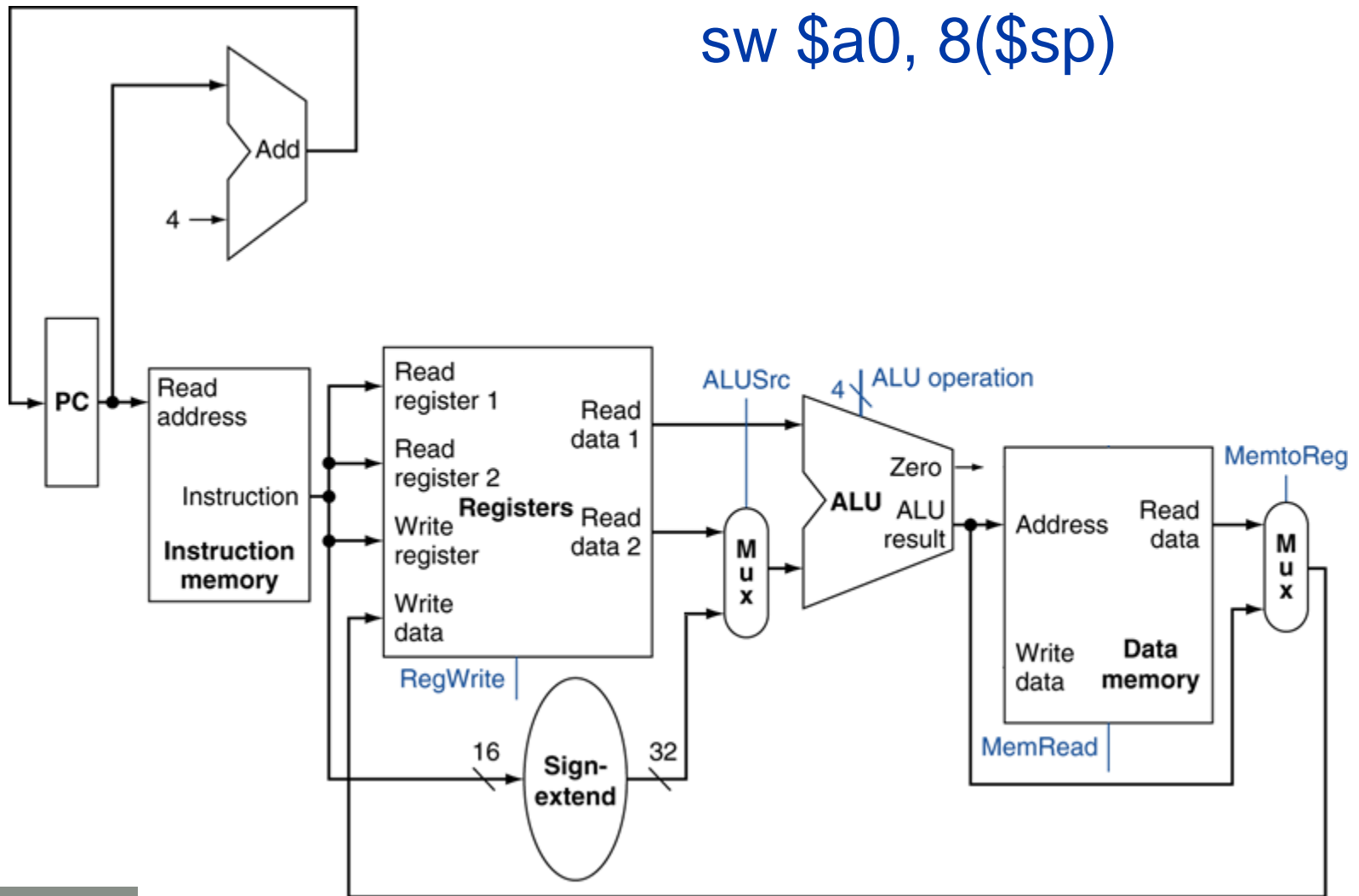
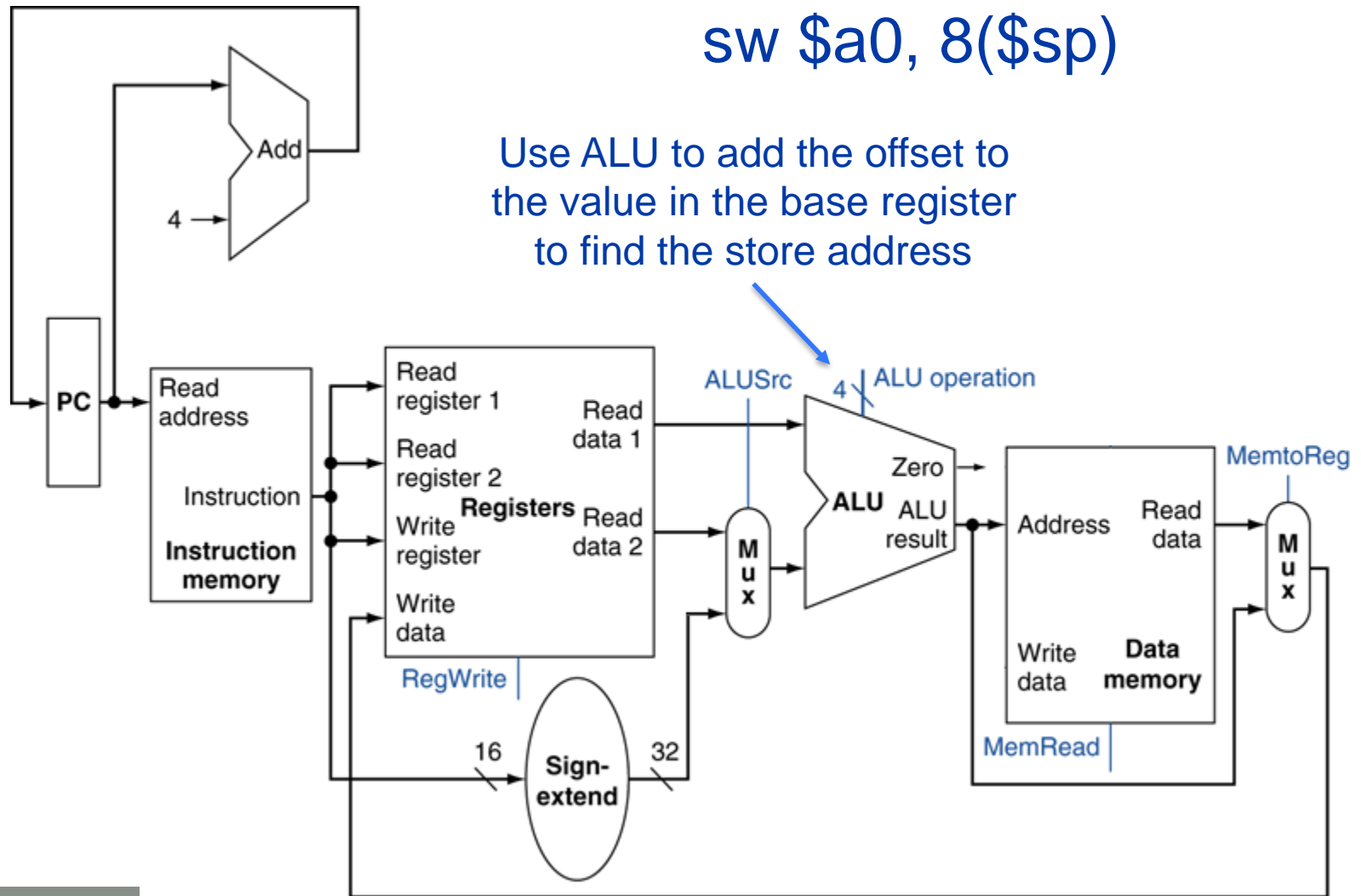
# Store Instructions

sw \$a0, 8(\$sp)


Use ALU to add the offset to the value in the base register to find the store address


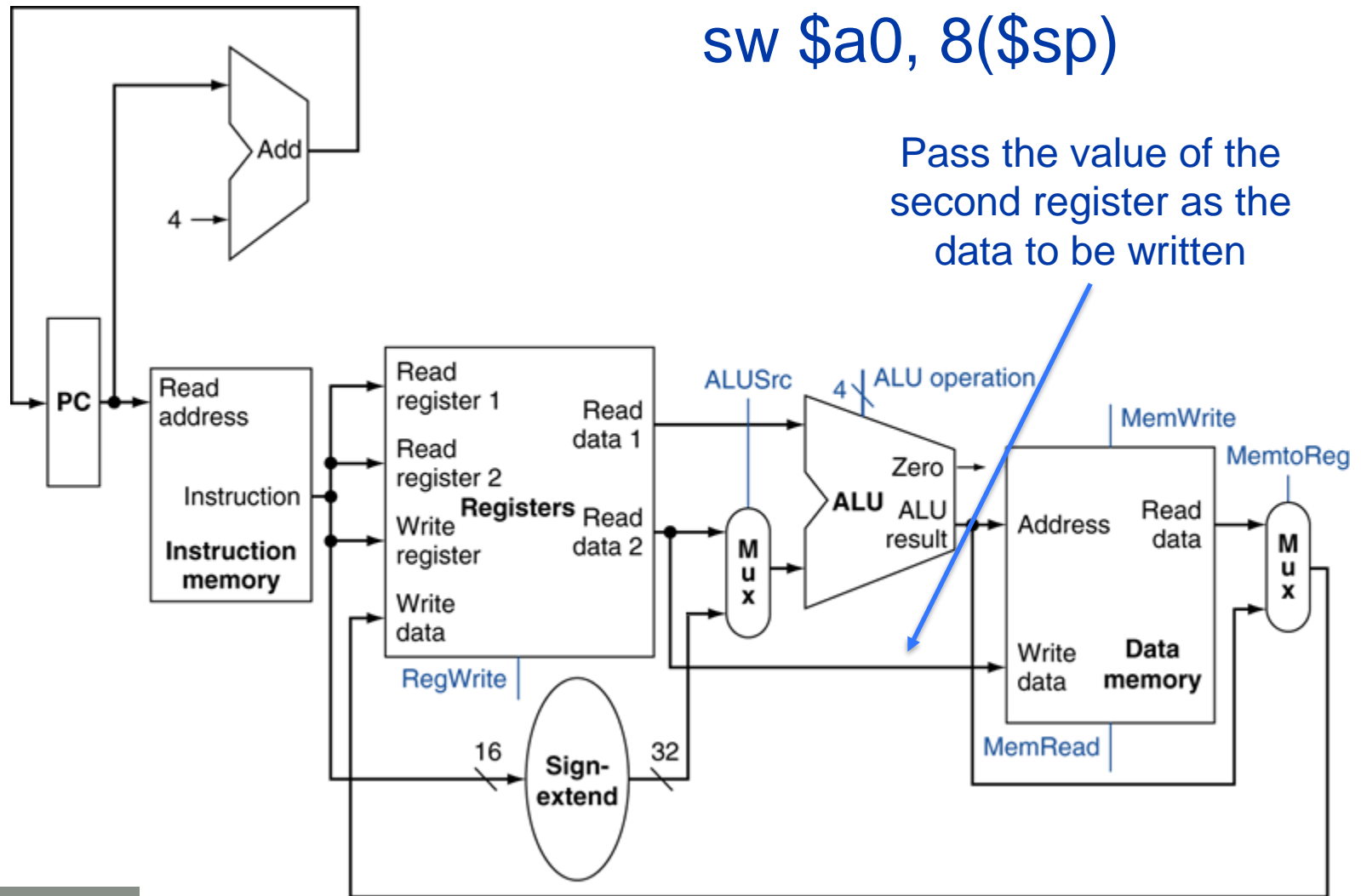
# Store Instructions

sw \$a0, 8(\$sp)


Pass the value of the second register as the data to be written





# Branch Instructions


beq \$t0, \$s0, offset

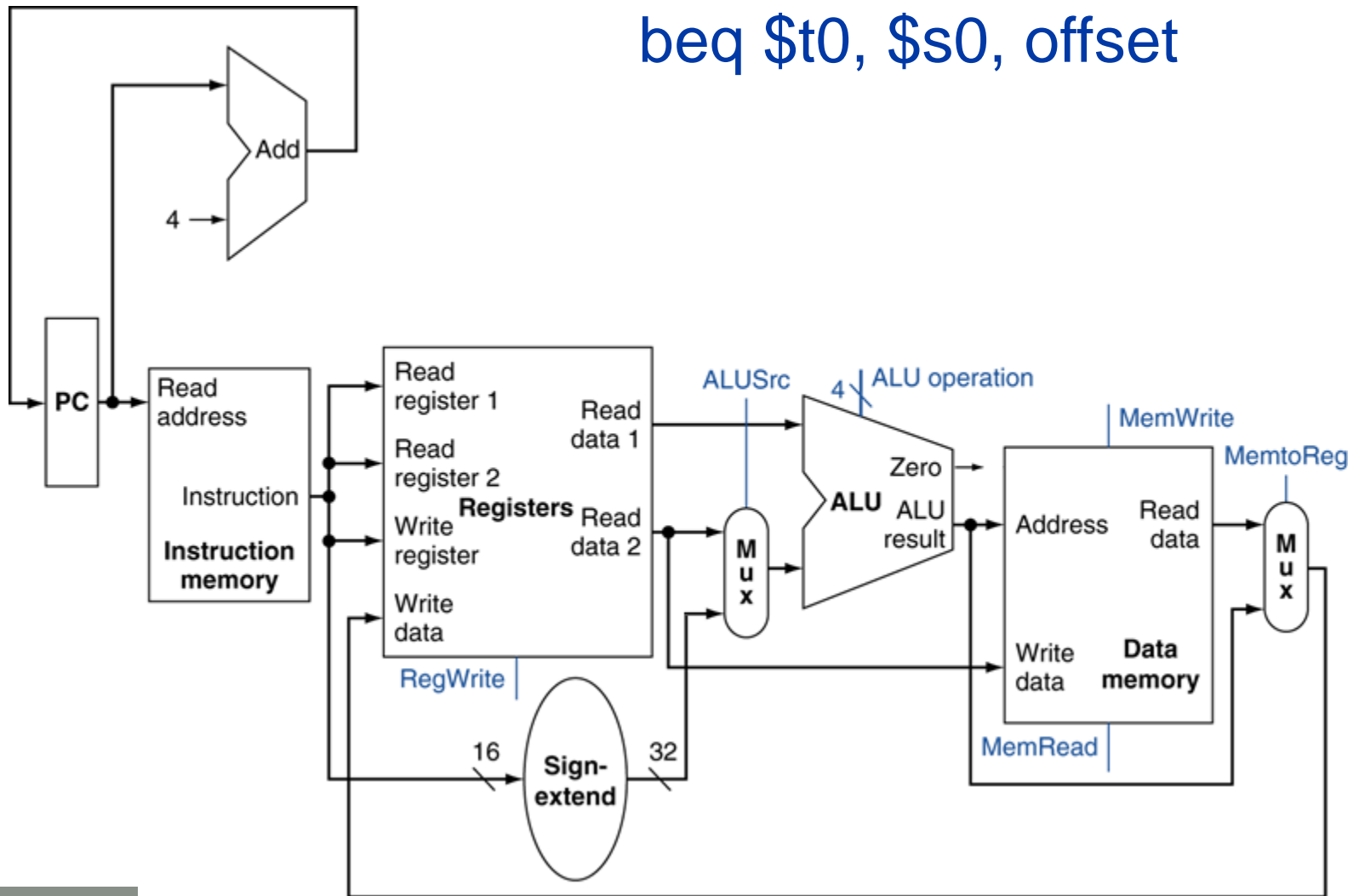
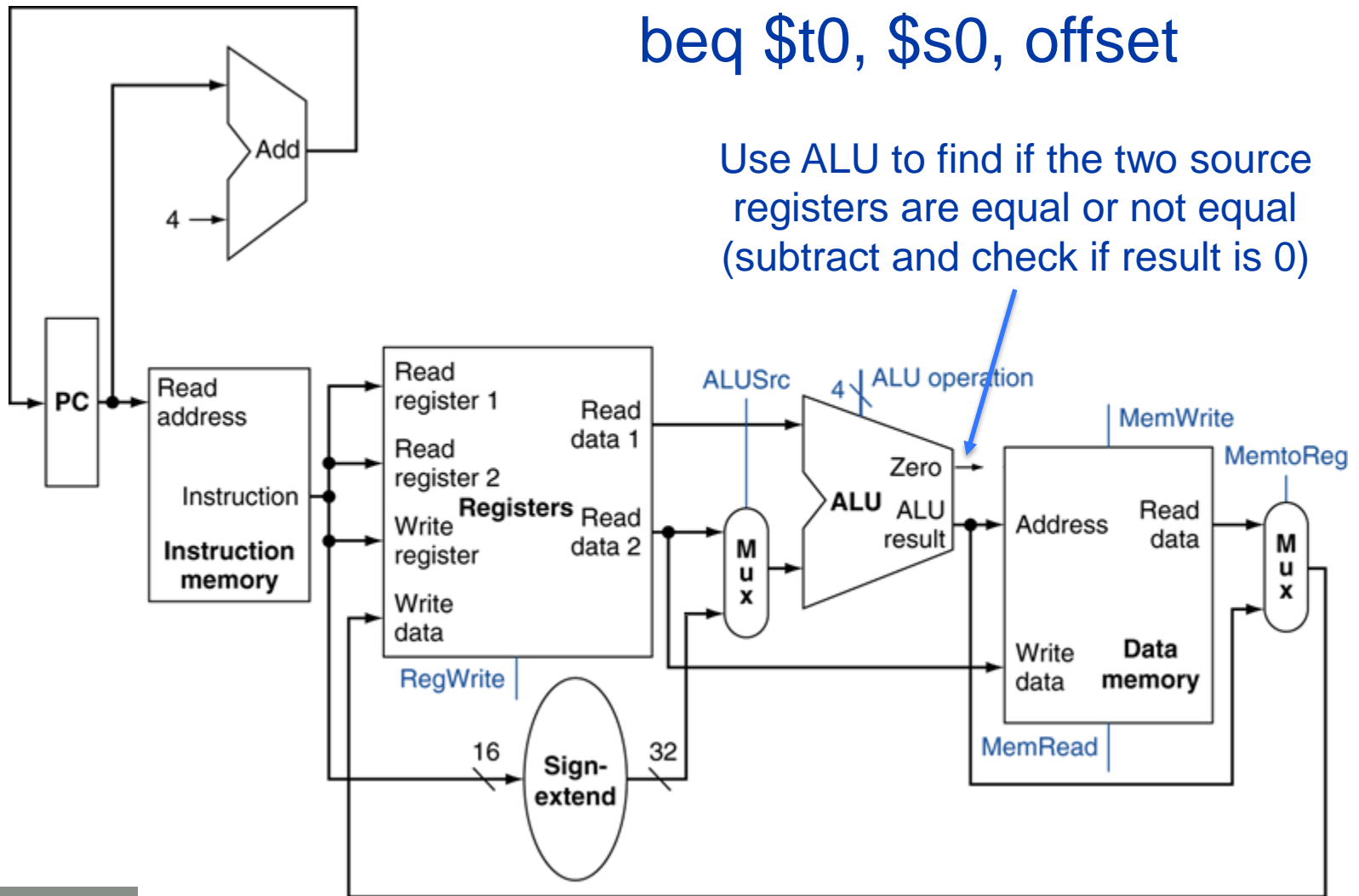
# Branch Instructions

beq \$t0, \$s0, offset


Use ALU to find if the two source registers are equal or not equal  
(subtract and check if result is 0)



 
# Branch Instructions

`beq $t0, $s0, offset`


Recall: Target address =  $PC + 4 + \text{offset} \times 4$




# Branch Instructions

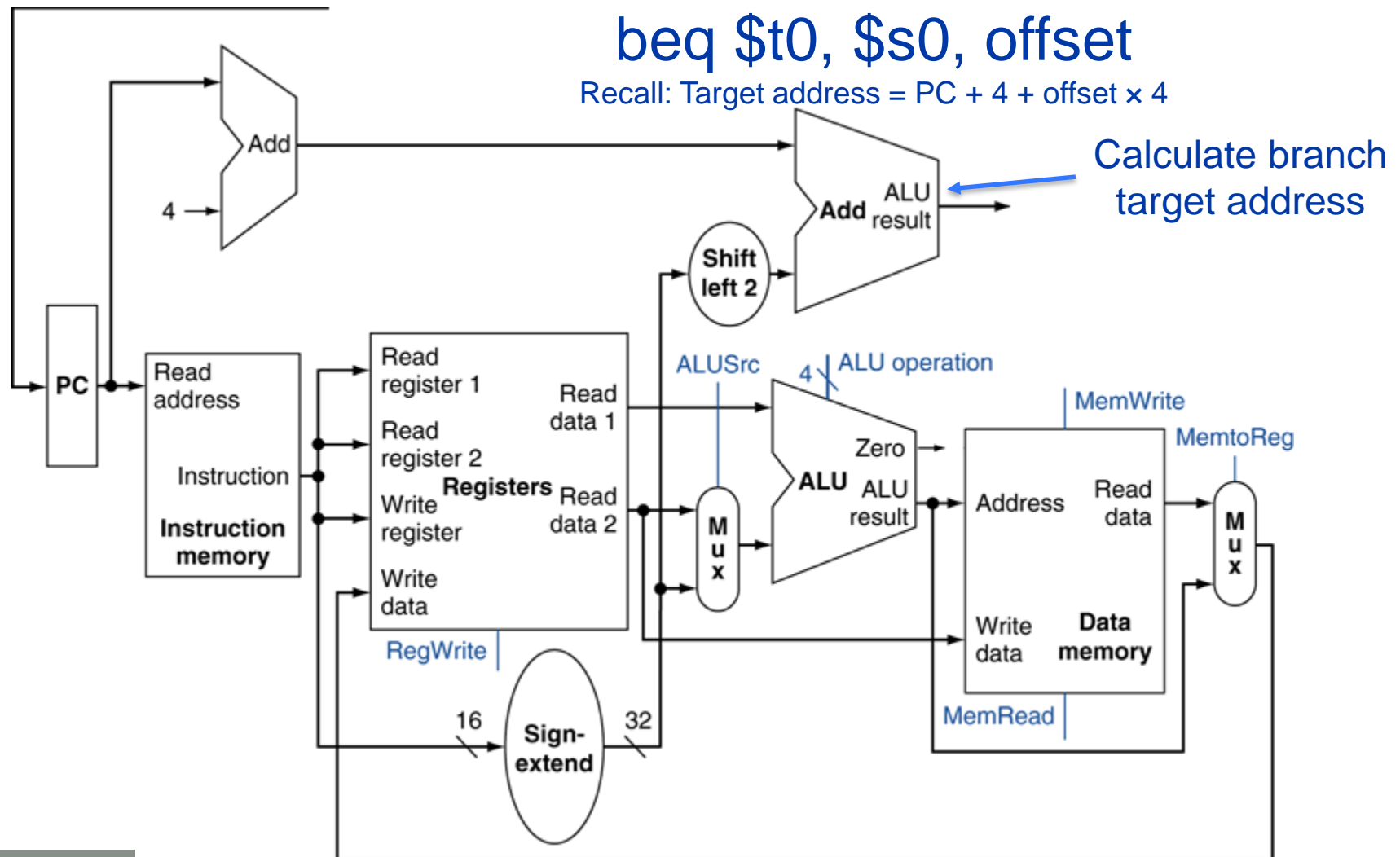

# Branch Instructions

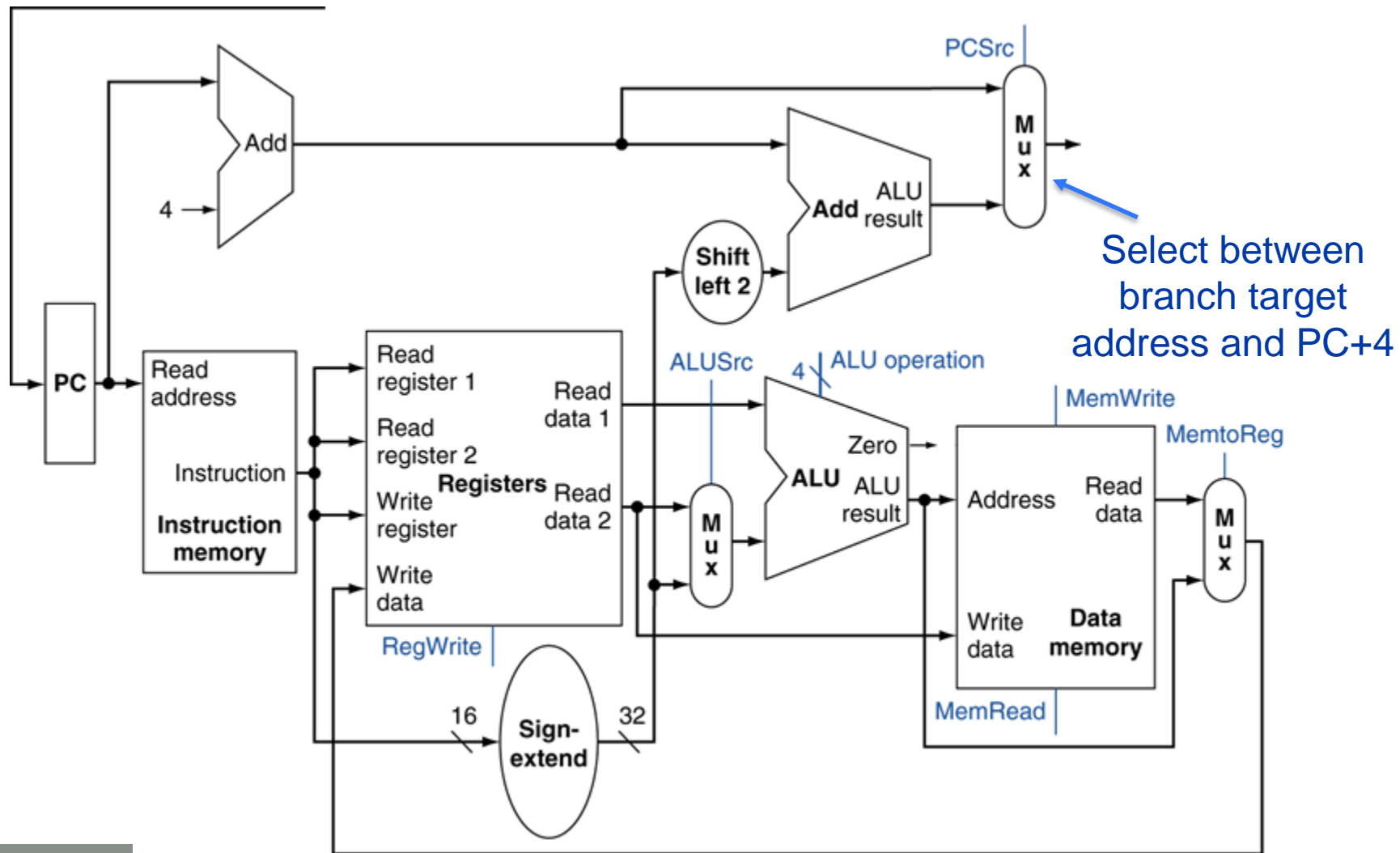

# Branch Instructions

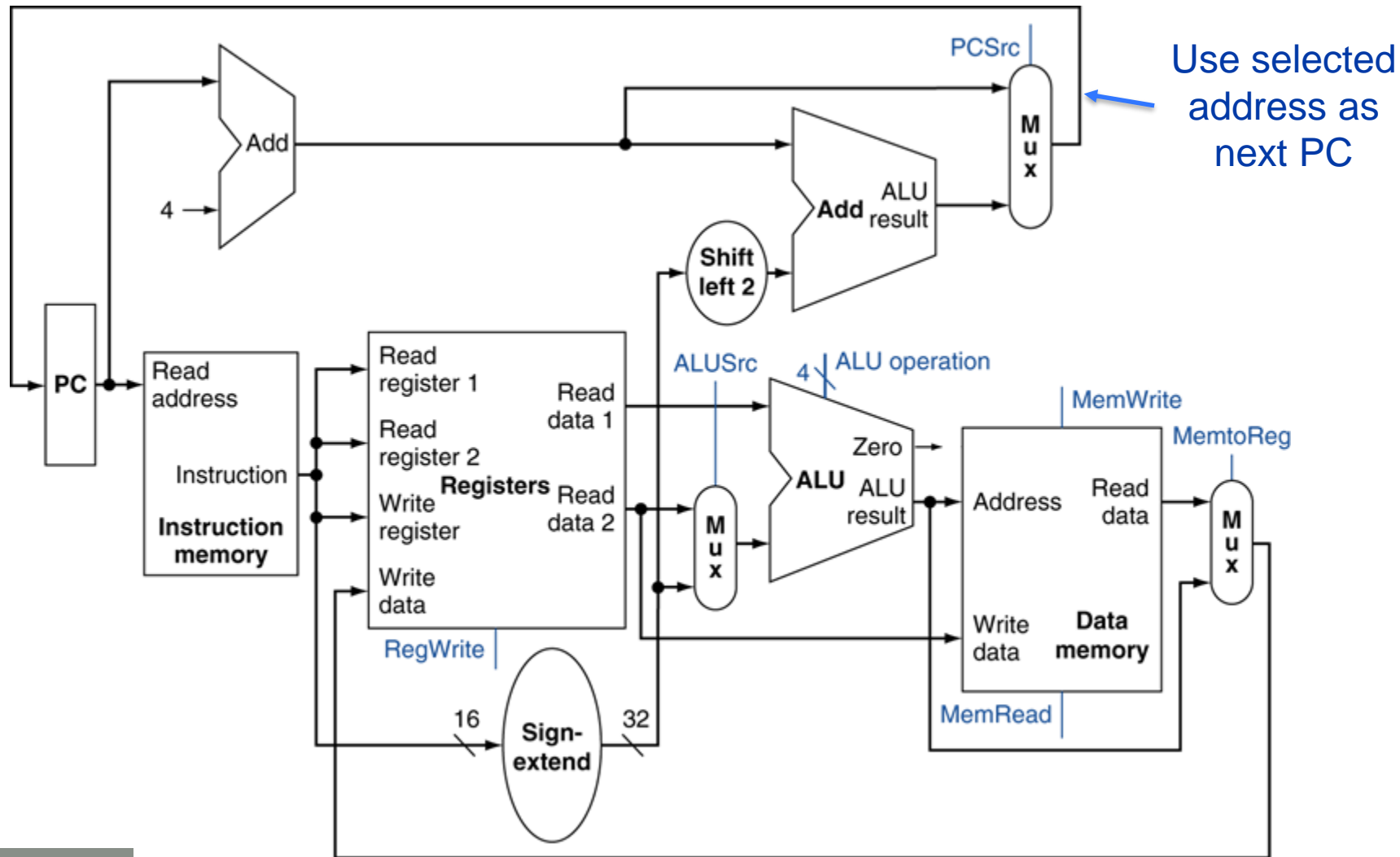

# Textbook Sections

- The content in these slides corresponds to:
  - Textbook:
    - *Computer Organization and Design, 5th Edition by David Patterson and John Hennessy, Morgan Kaufmann, 2014.*
  - Sections:
    - 4.1, 4.3