 


Lecture 22: Datapath Control Signals

CMPS 221 – Computer Organization and Design

Last Time: Building a Datapath




Introduction

- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - A simplified version
 - A more realistic pipelined version
- Focus on a simple subset (shows most aspects)
 - Arithmetic/logical: add, sub, addi, slt
 - Memory reference: lw, sw
 - Control transfer: beq, j


Building a Datapath

- A **datapath** is a set of elements that process data and addresses in the CPU
- Components of a MIPS datapath:
 - PC register, instruction memory (fetch instructions)
 - Register file (read/write registers)
 - ALUs:
 - Arithmetic/logic operations
 - Memory address for load/store
 - Branch target address
 - Data memory (load/store data)


Full Datapath

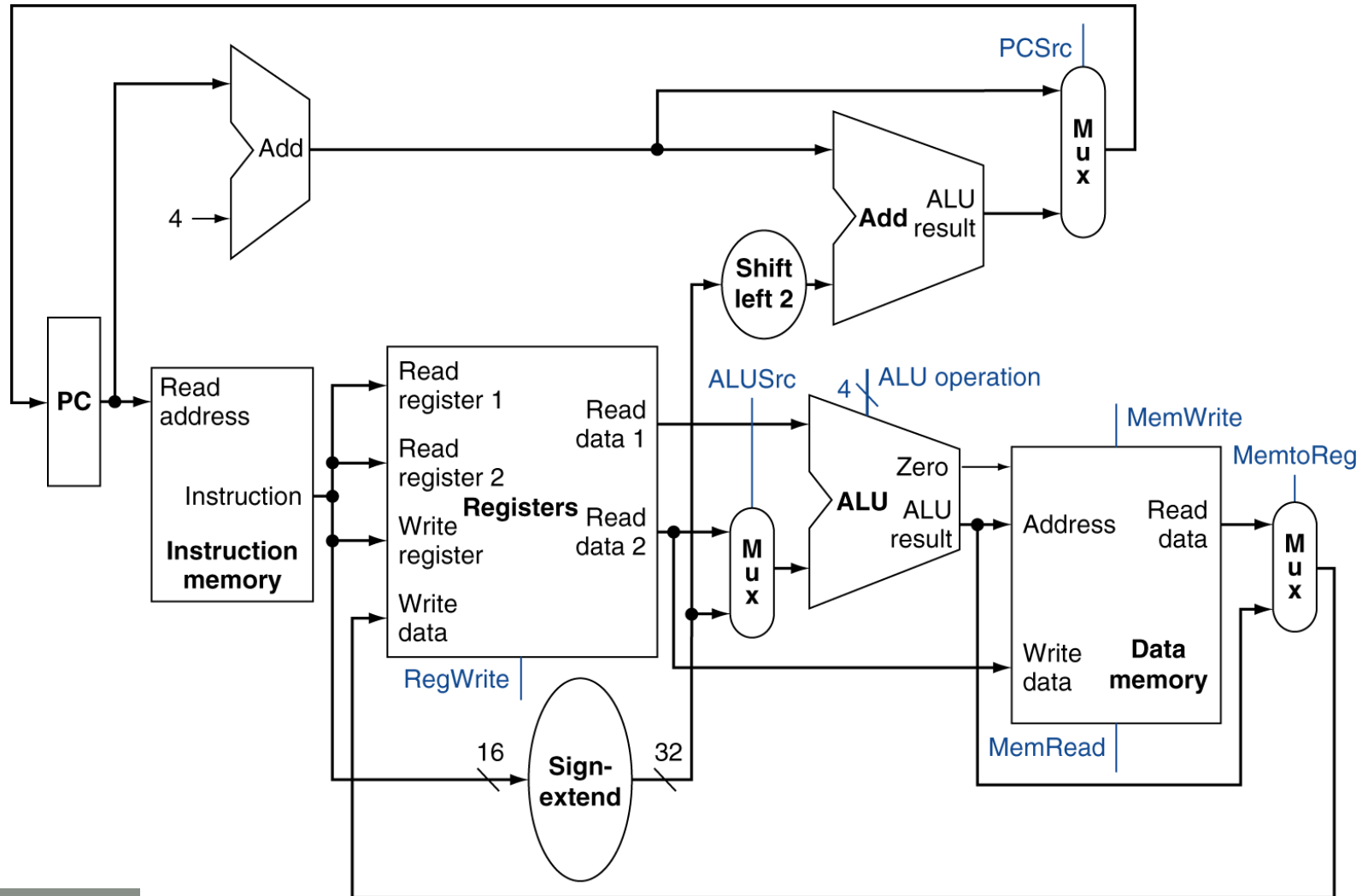

Today: Datapath Control Signals

 


Instruction Fetch

 

Instruction is 32 bits
which will be used to
determine the execution


R-type Instructions

 


R-type

| op | rs | rt | rd | shamt | funct |
|-------|-------|-------|-------|-------|-------|
| 31-26 | 25-21 | 20-16 | 15-11 | 10-6 | 5-0 |

R-type Instructions

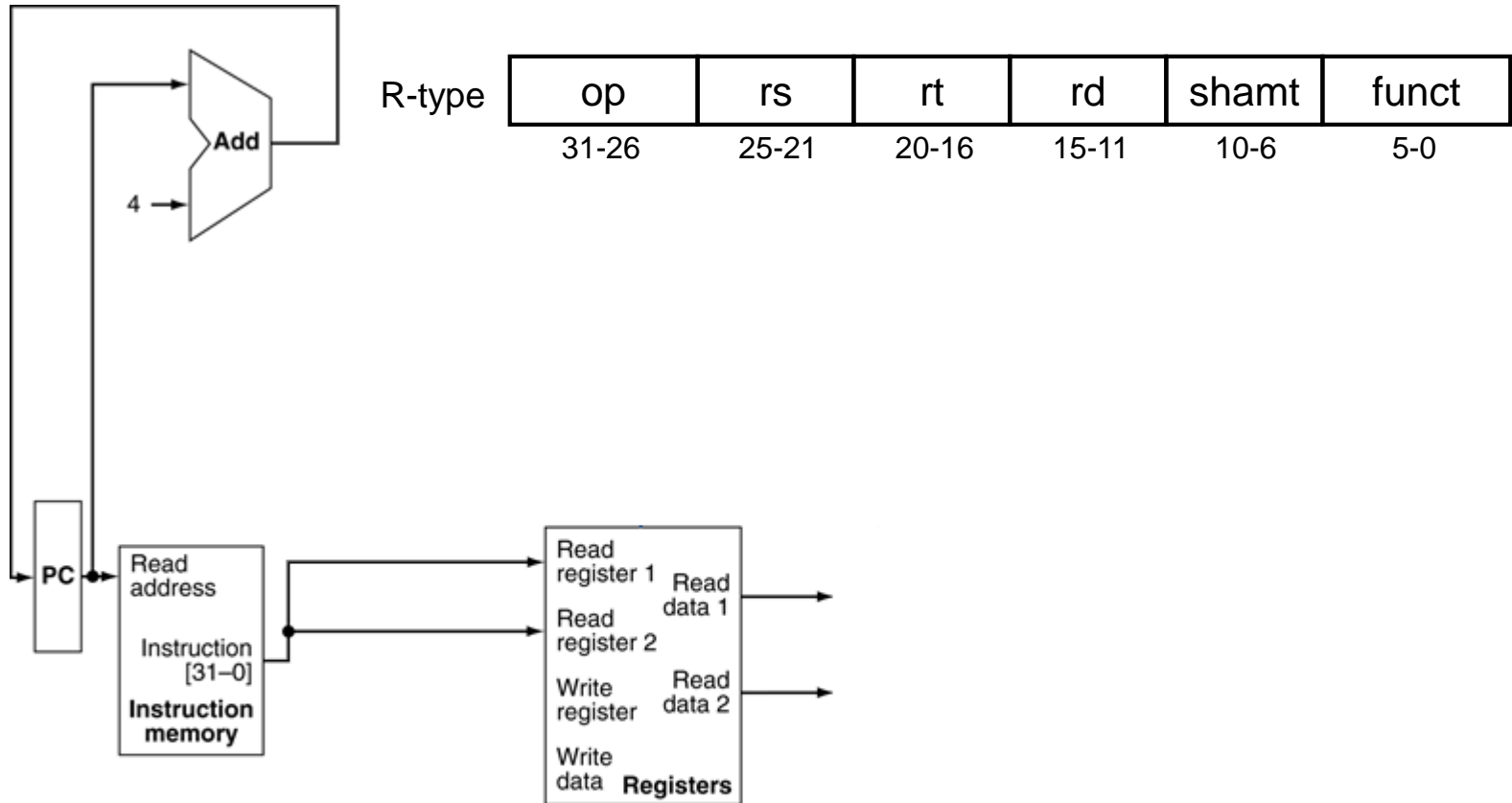


R-type Instructions

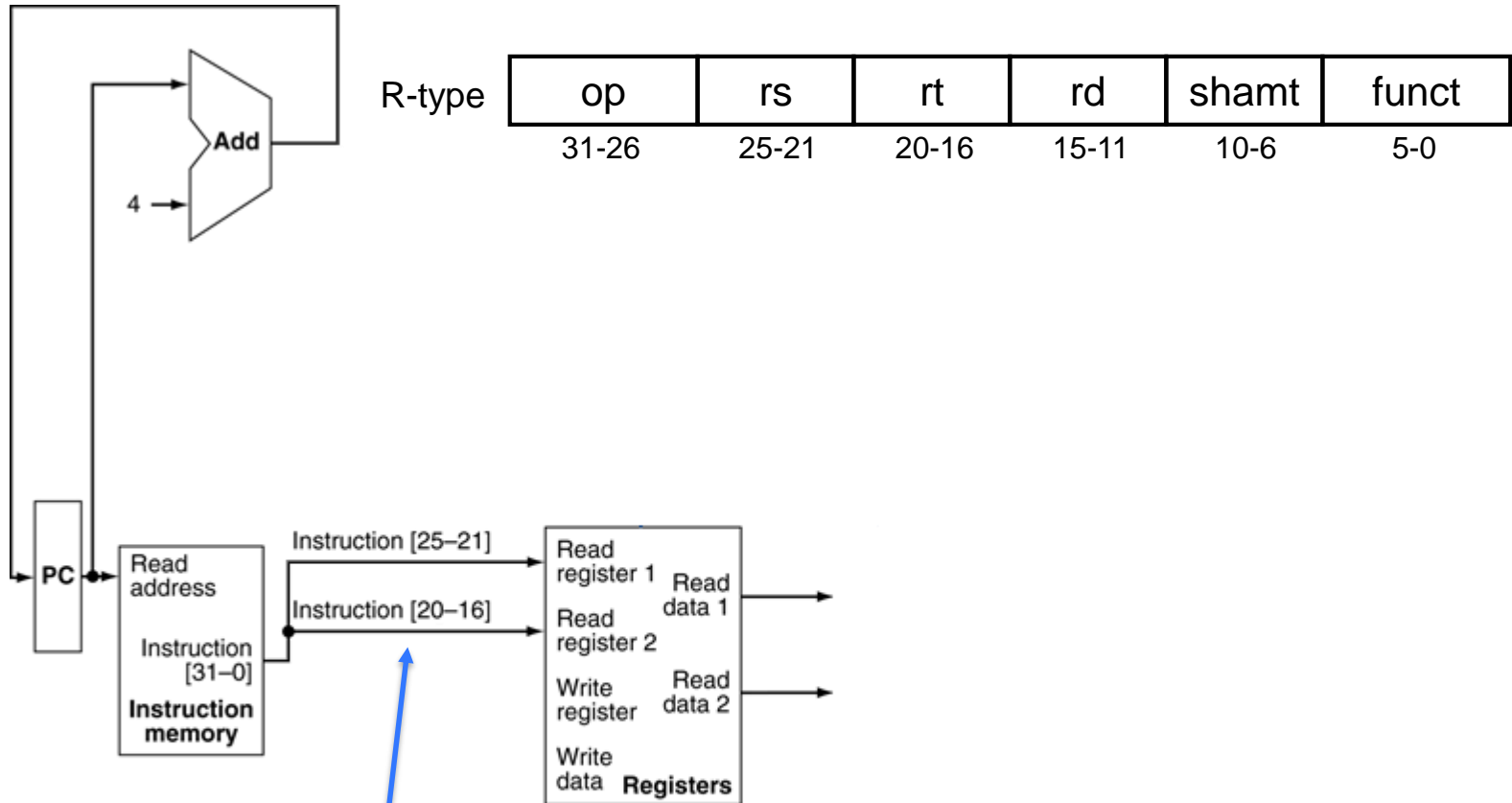


Source register
numbers extracted
from rs and rt bits

R-type Instructions

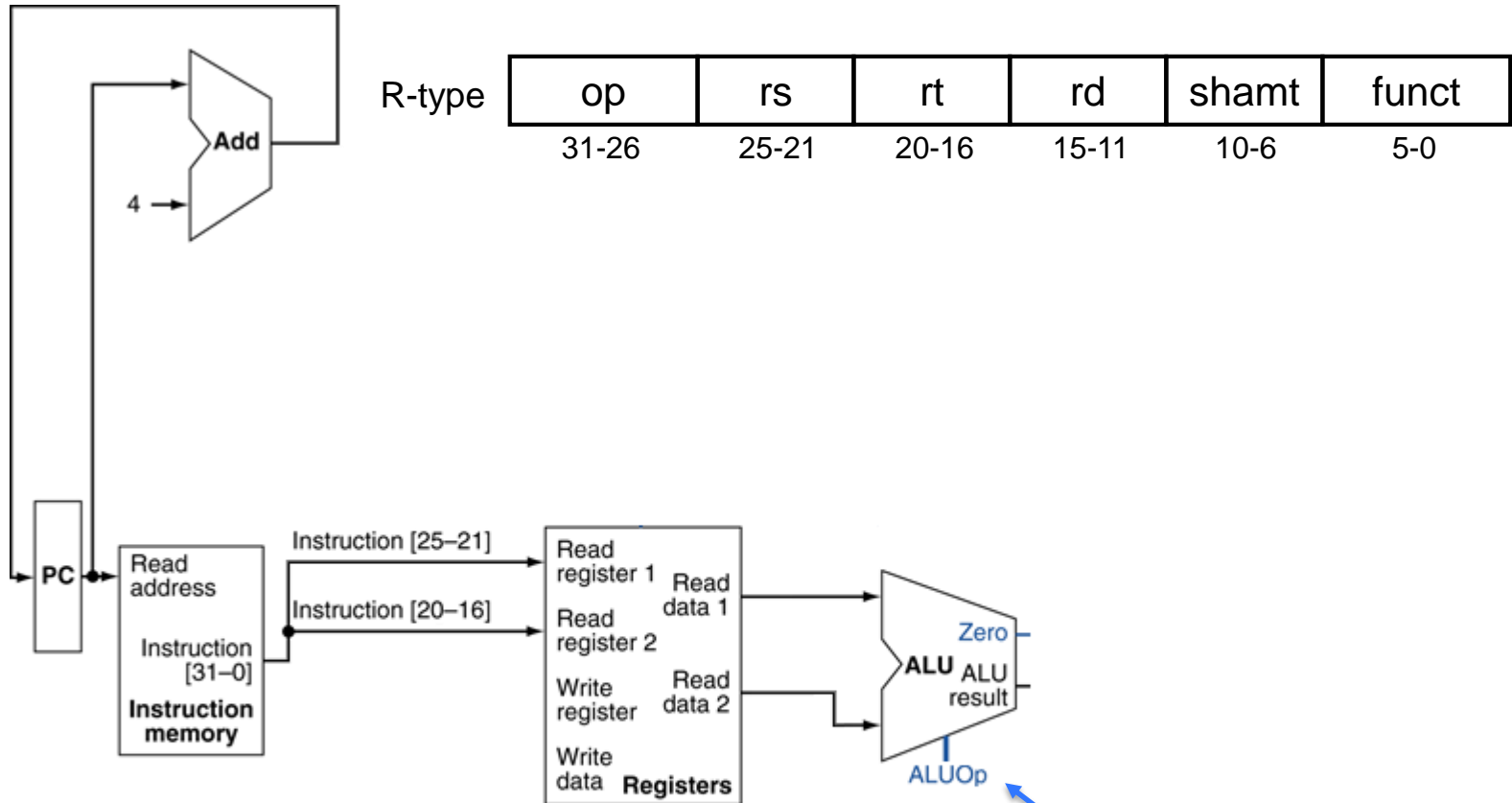


ALUOp specifies
the operation done
by the ALU


R-type Instructions

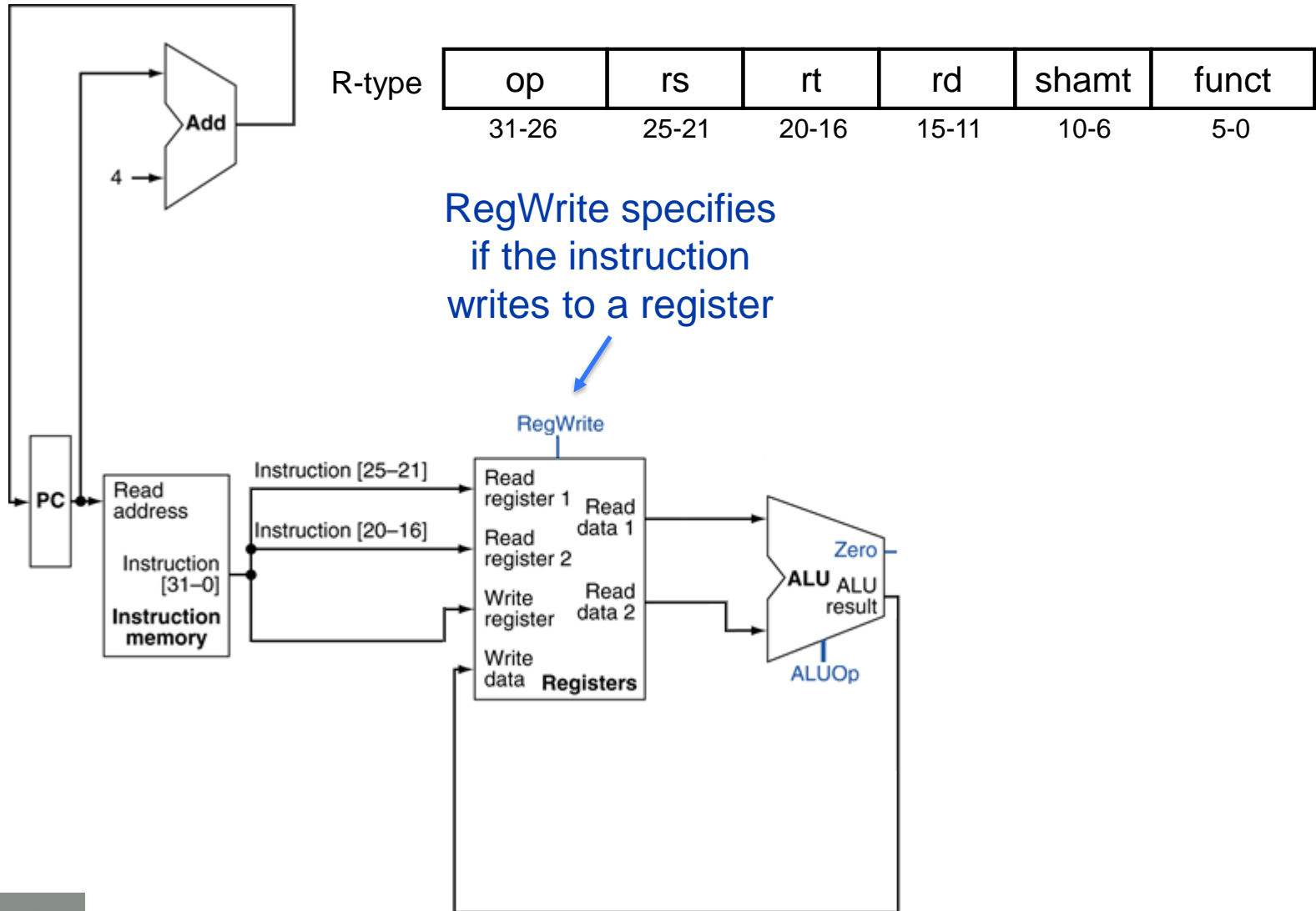


R-type Instructions

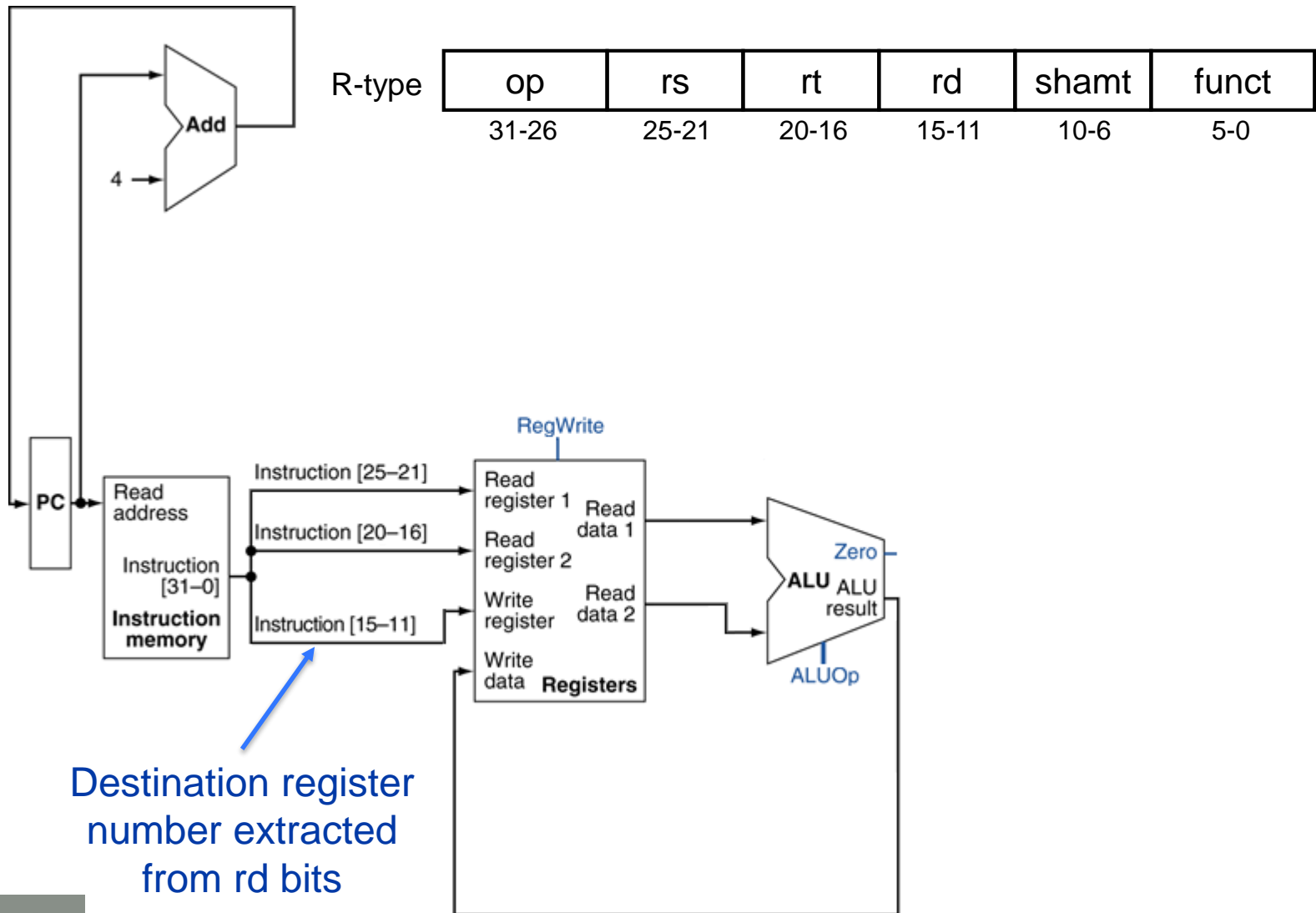


Immediate Instructions

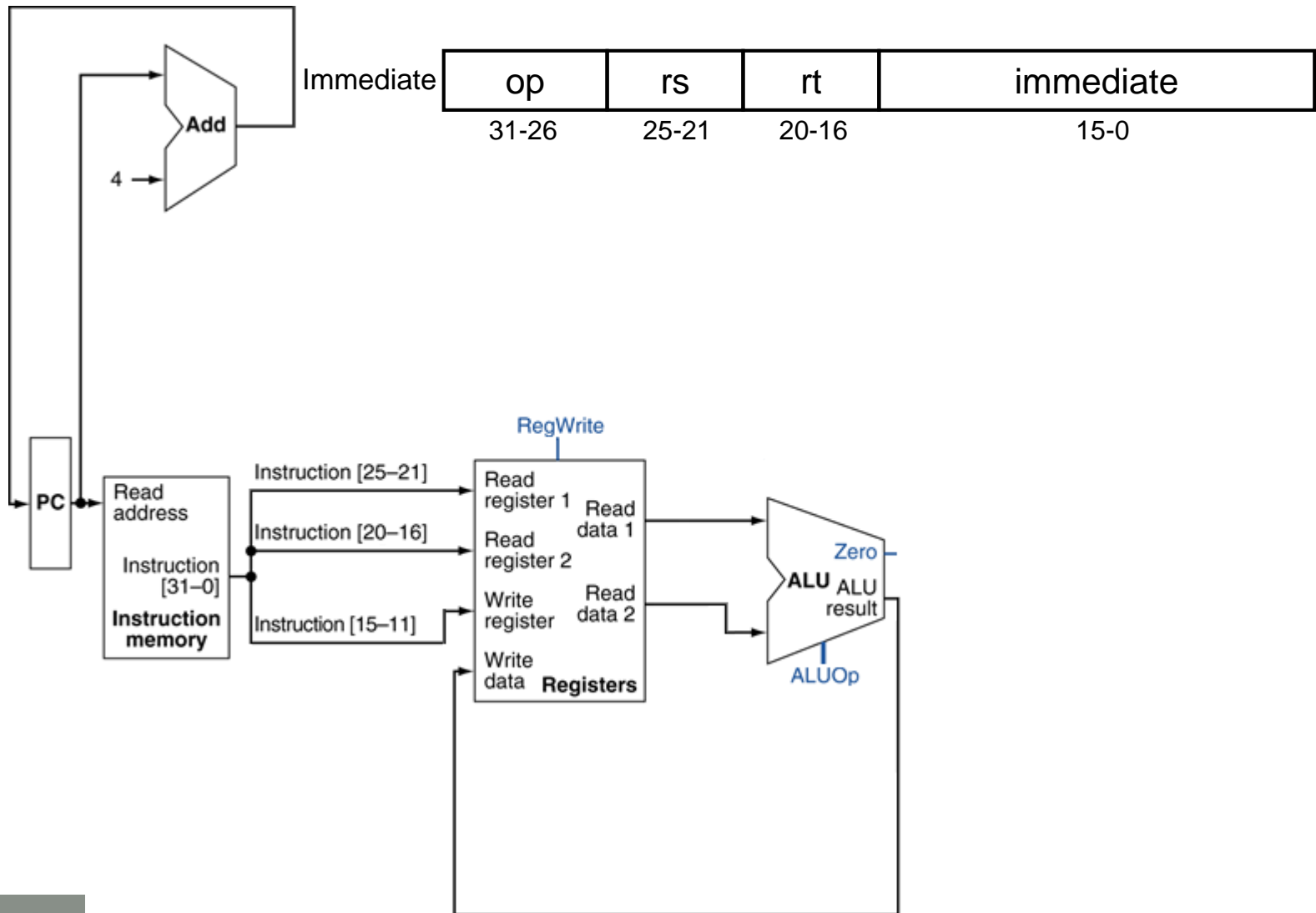


Immediate Instructions

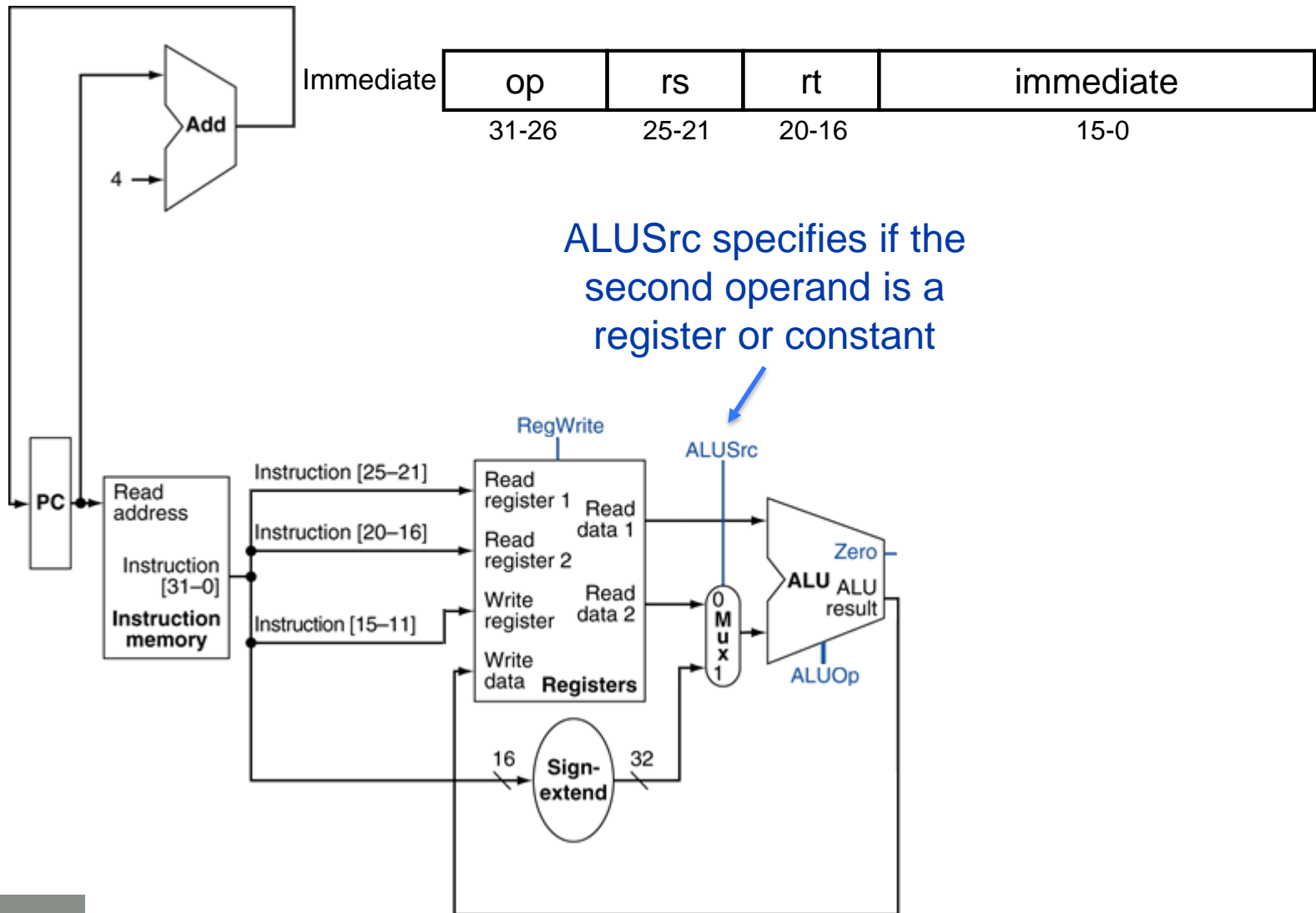


Immediate Instructions

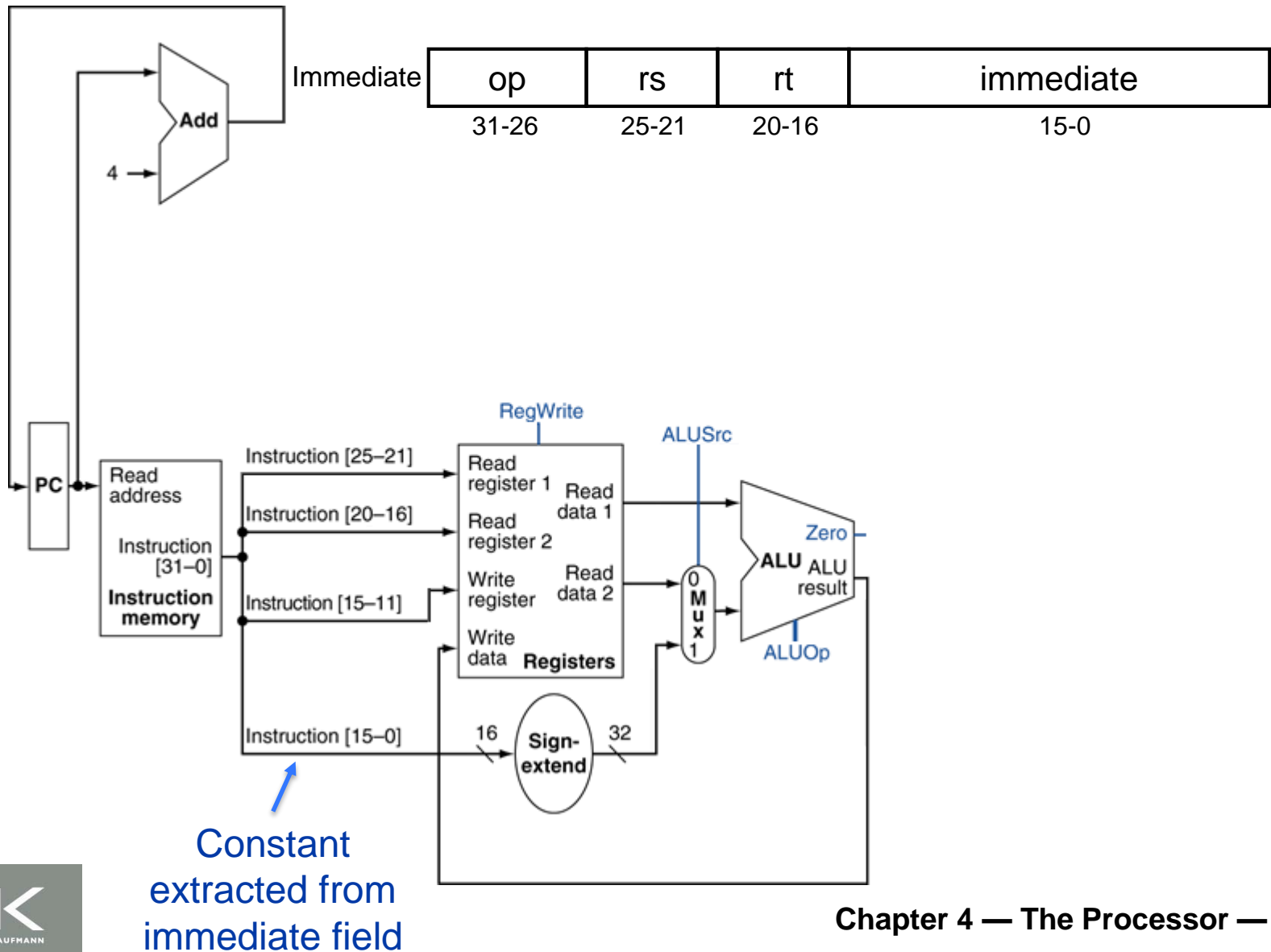


Immediate Instructions

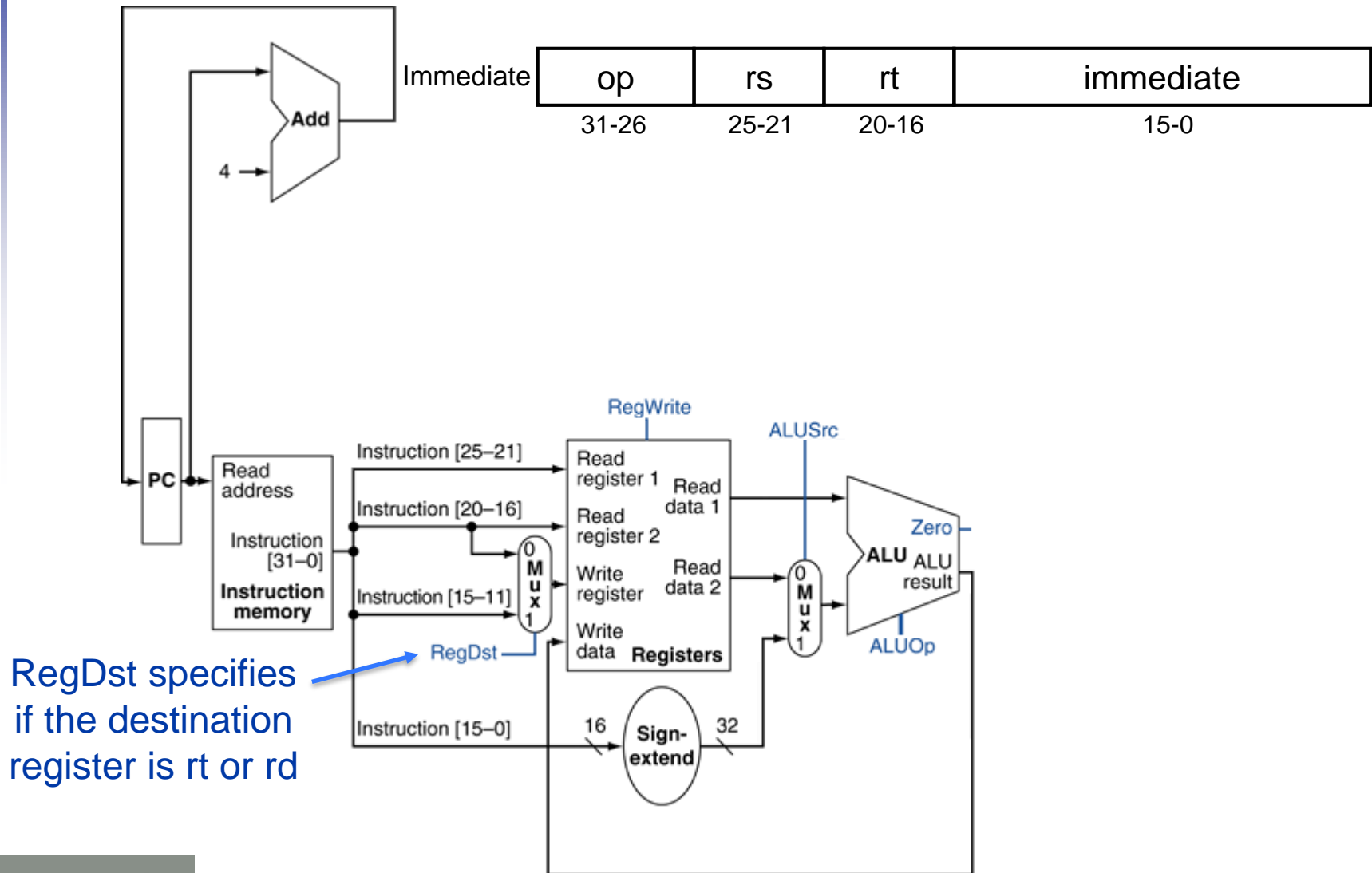


Load Instructions

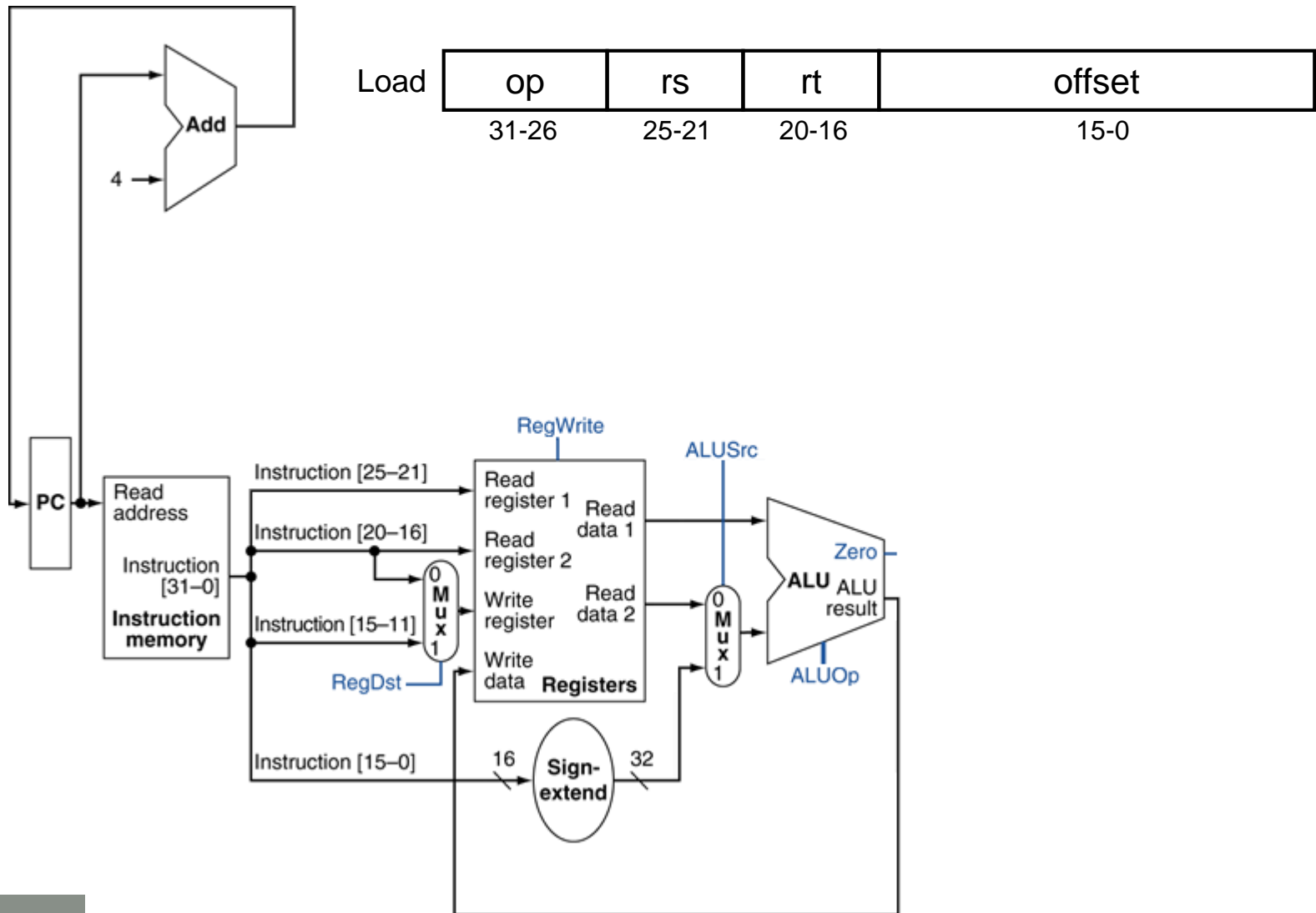


Load Instructions

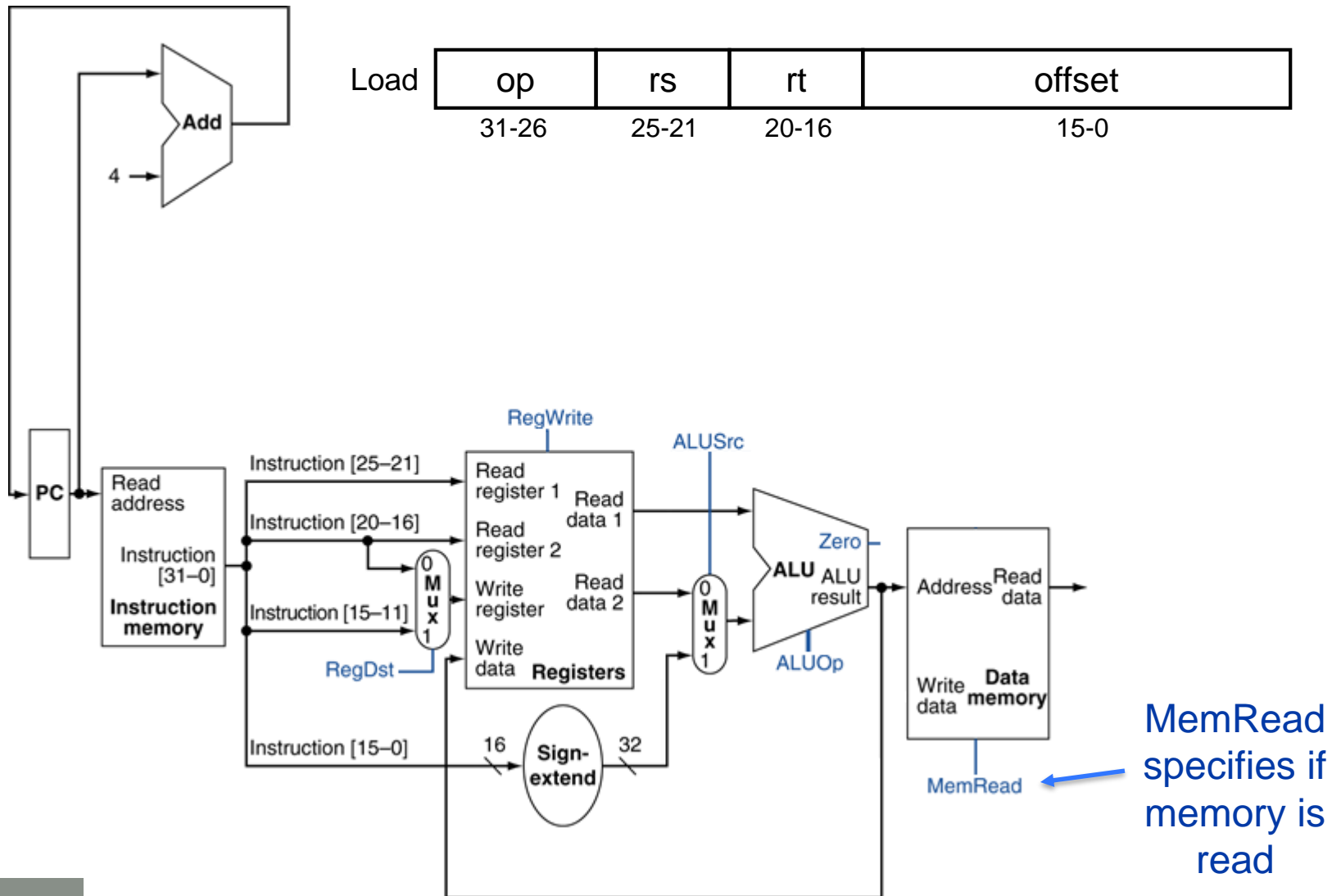


Load Instructions

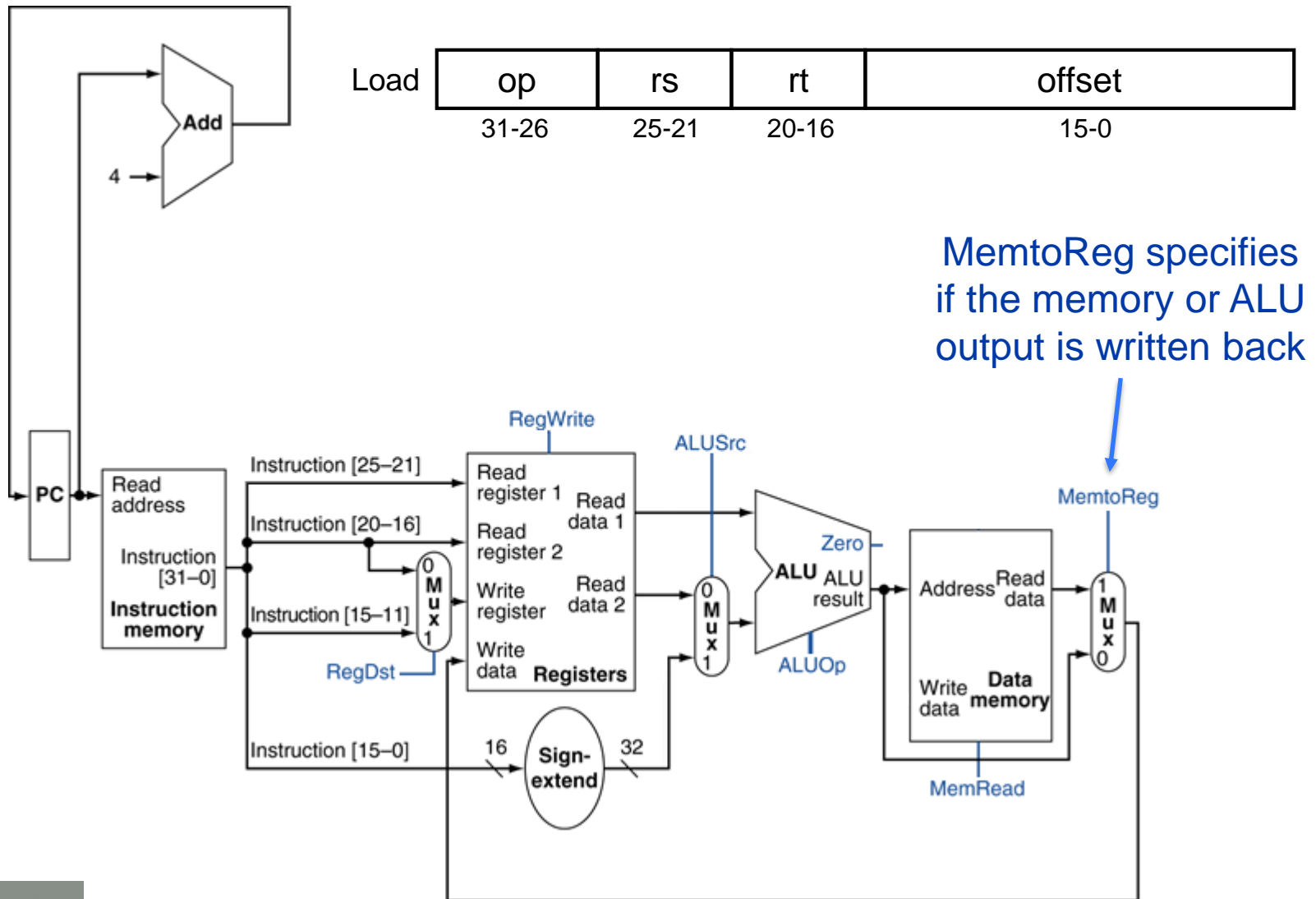


Store Instructions

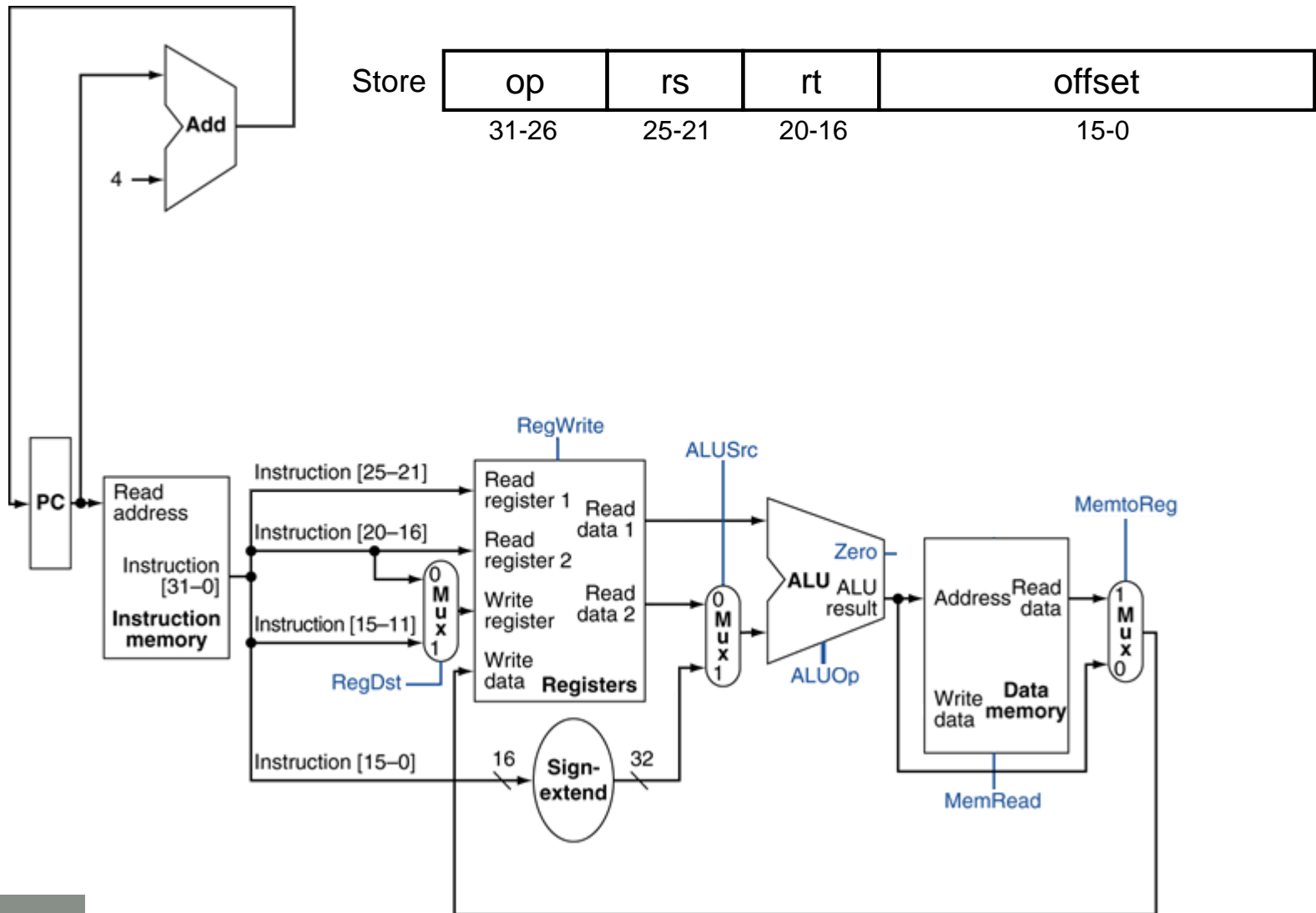


Store Instructions

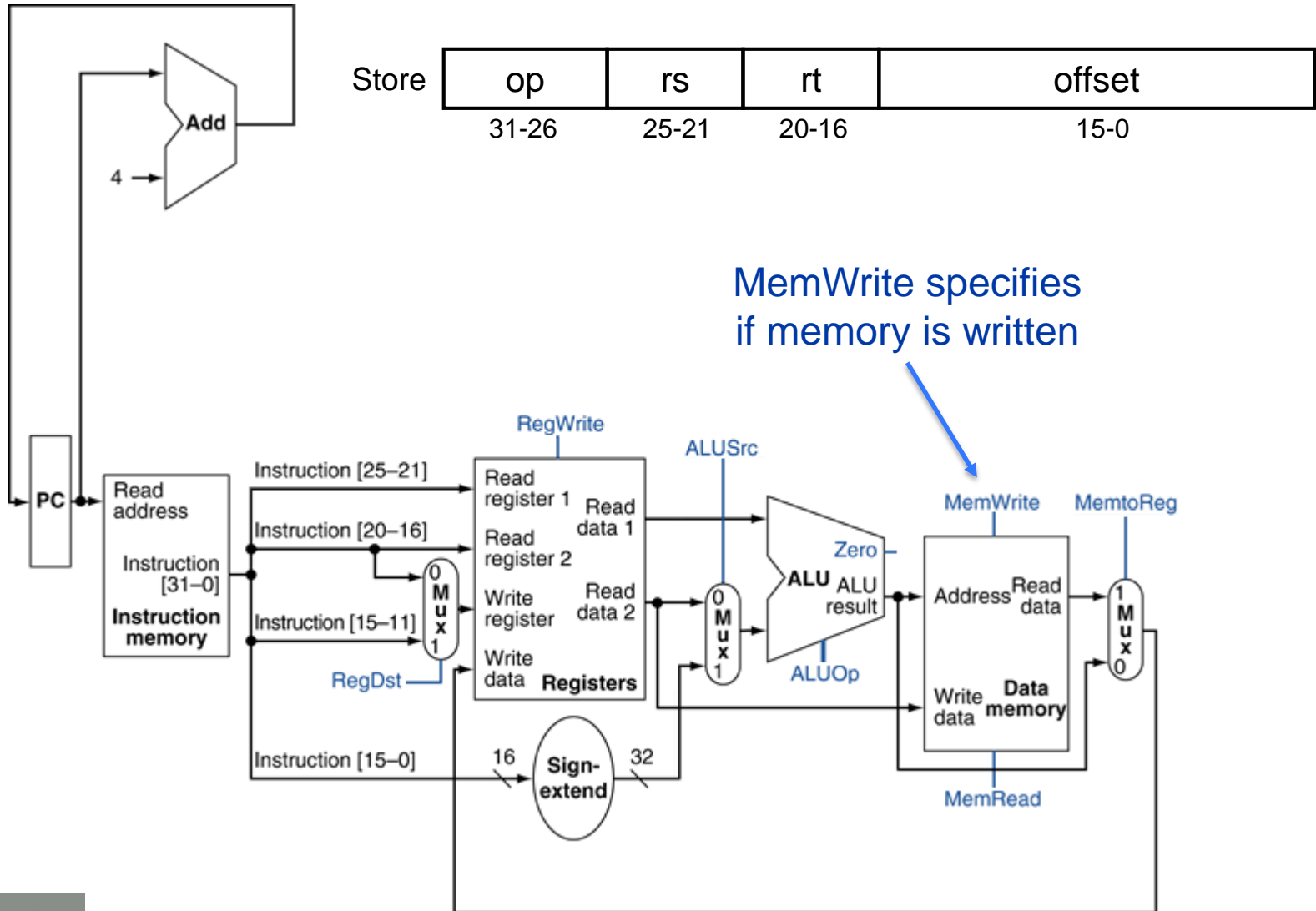

Branch Instructions

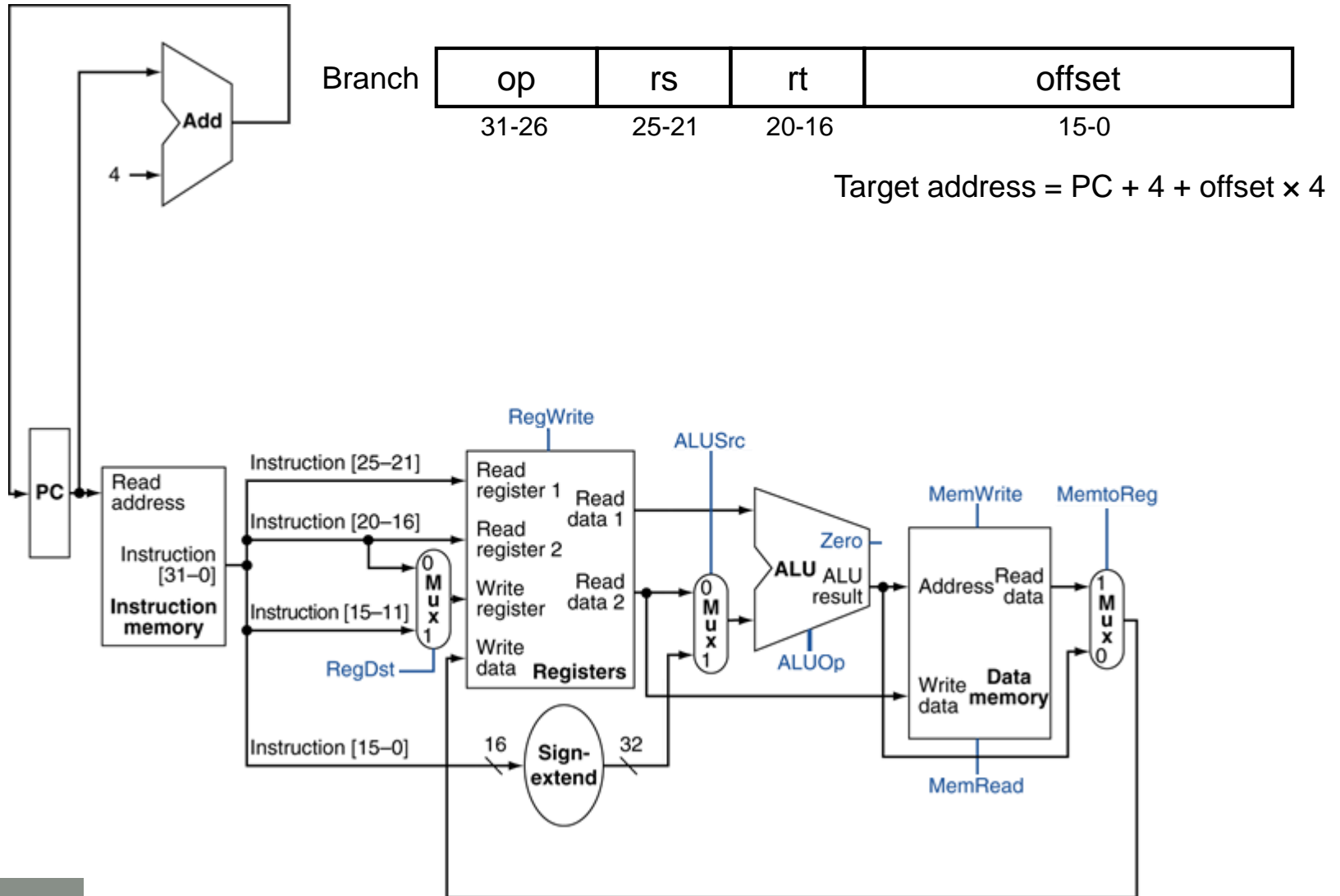


Branch Instructions

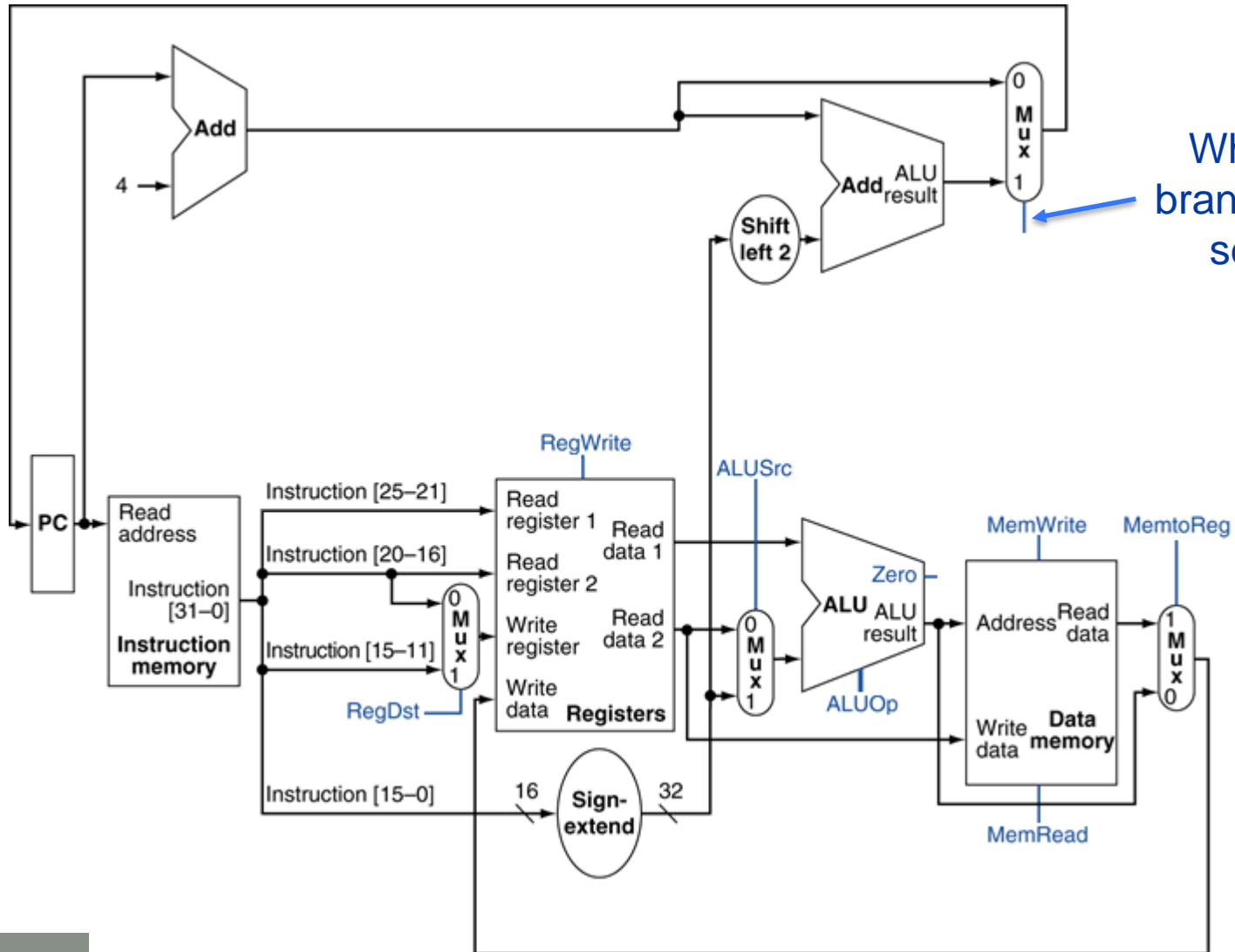

When is the branch address selected?


Branch Instructions

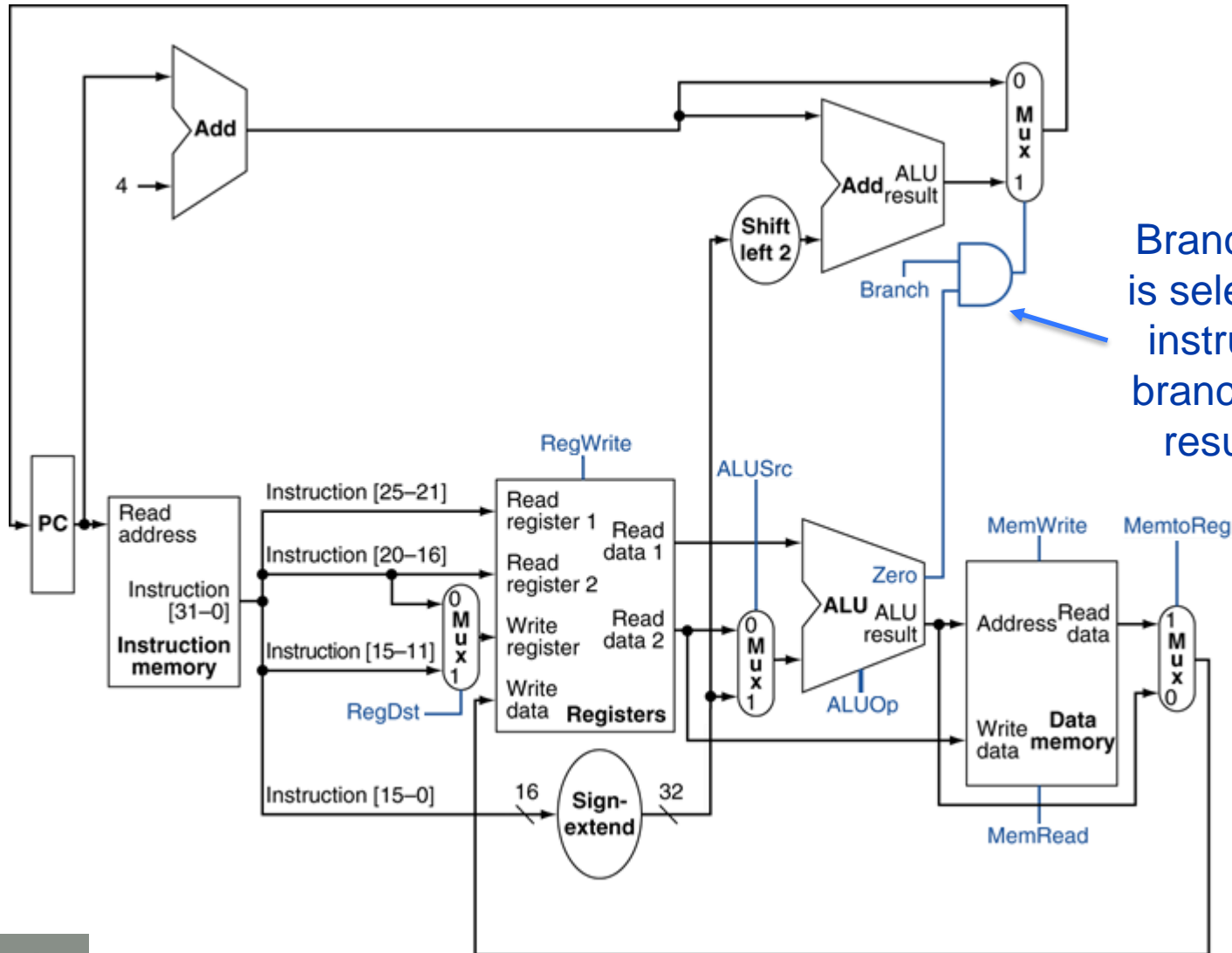

Branch address is selected when instruction is a branch and ALU result is zero


How to determine all the control signals?

Main Control Unit

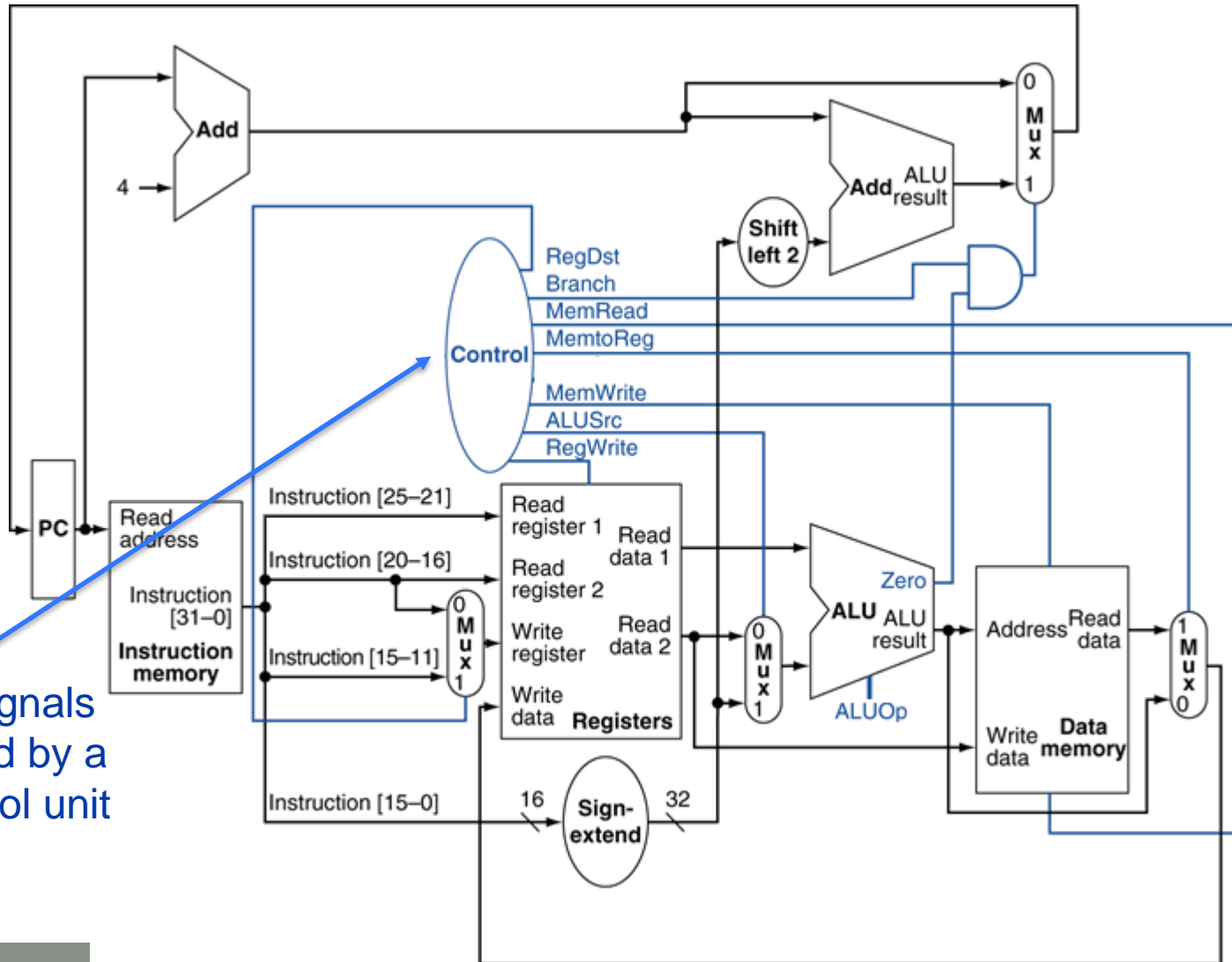


Control signals
determined by a
main control unit


Main Control Unit

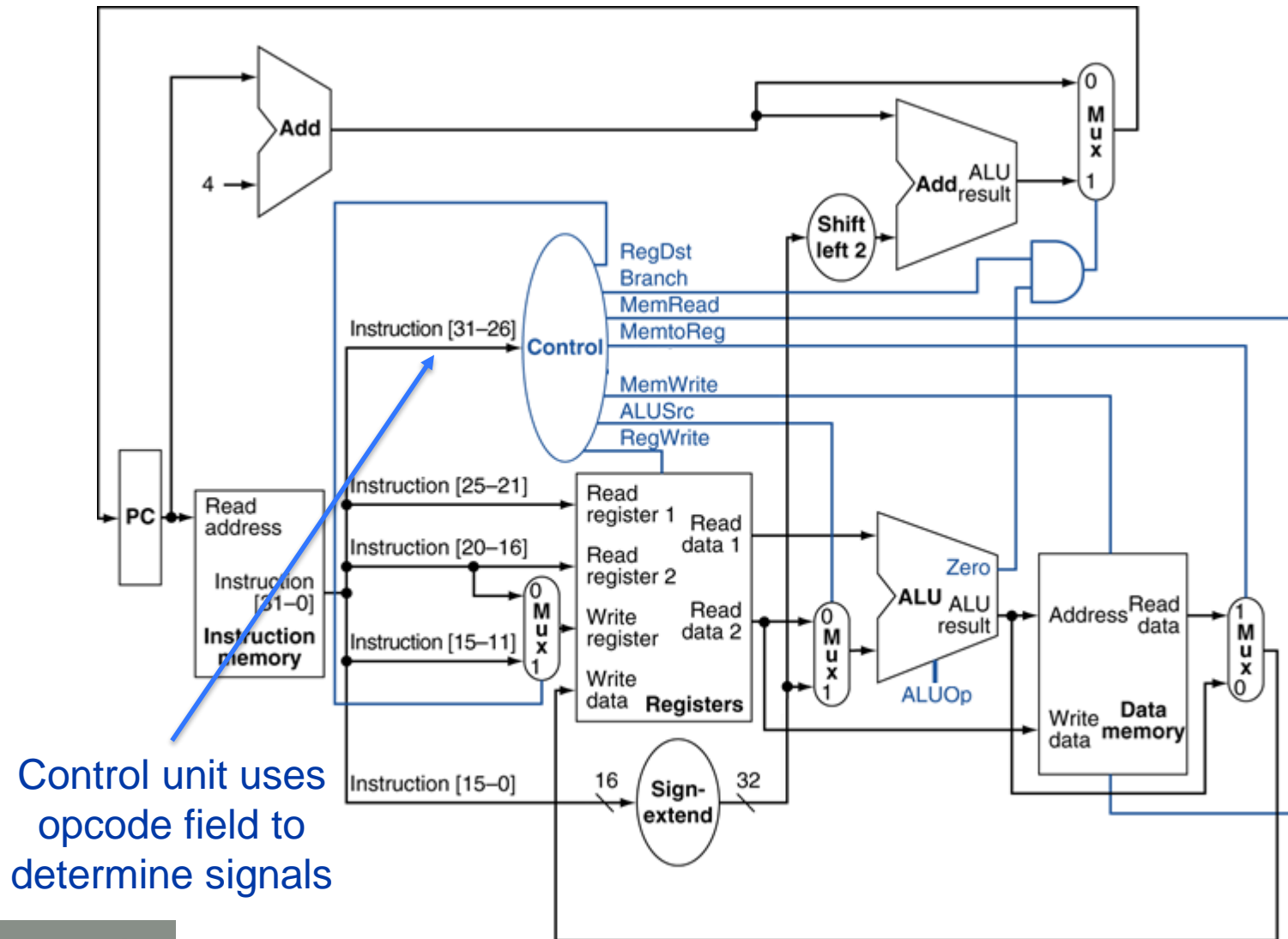


ALU Control Unit

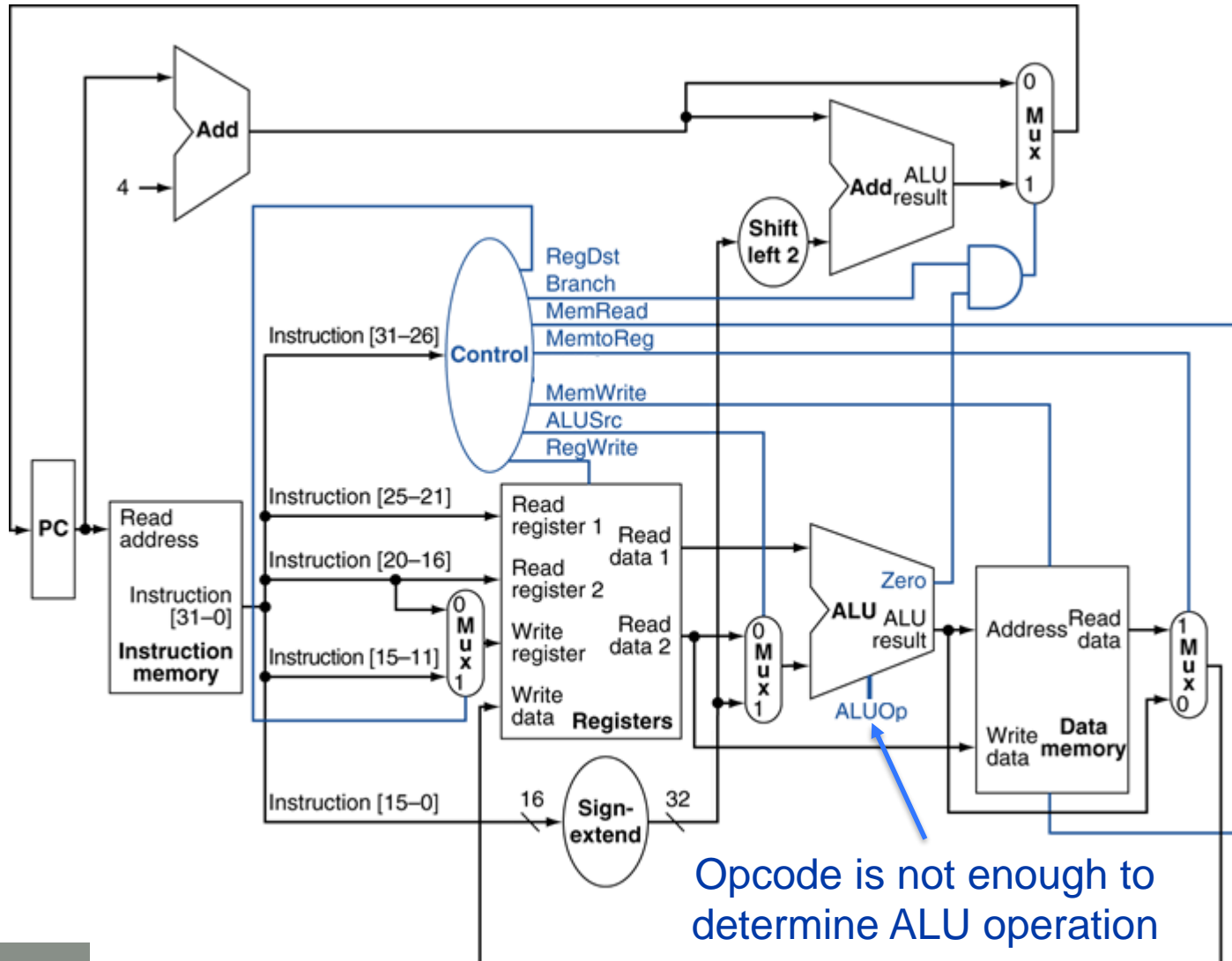

ALU Control Unit

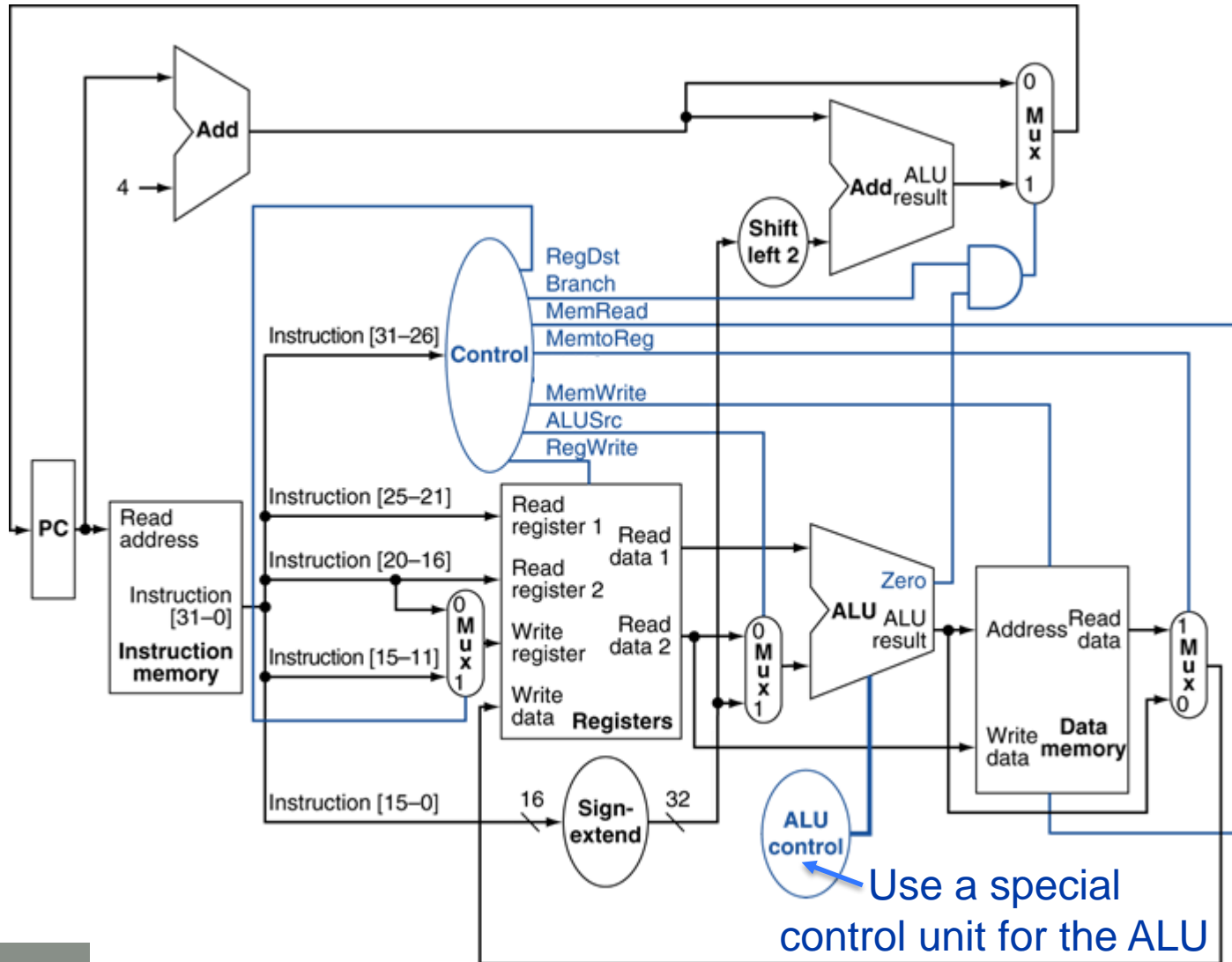


ALU Control Unit

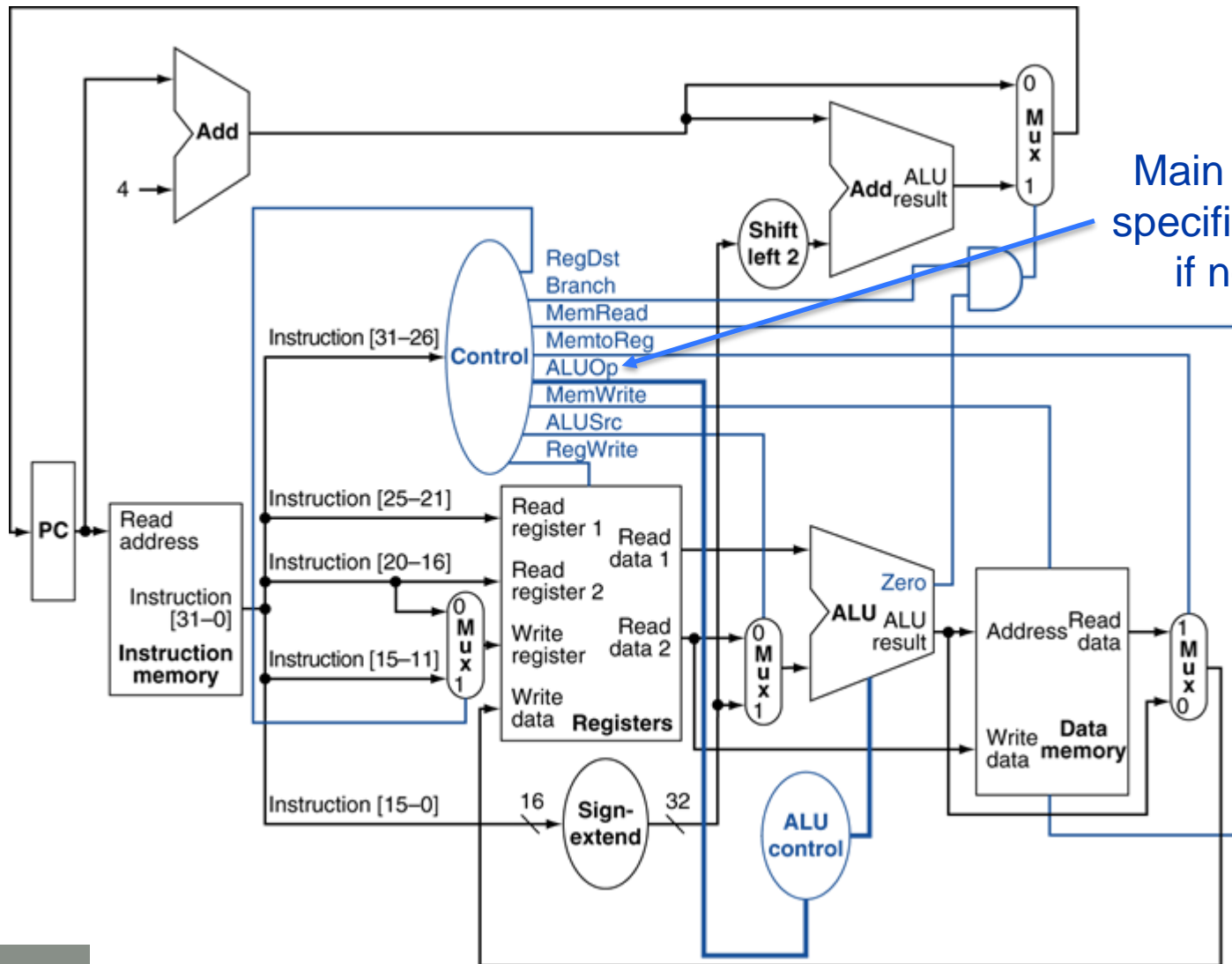

Funct field
 specifies operation
 if R-type





Jump Instructions

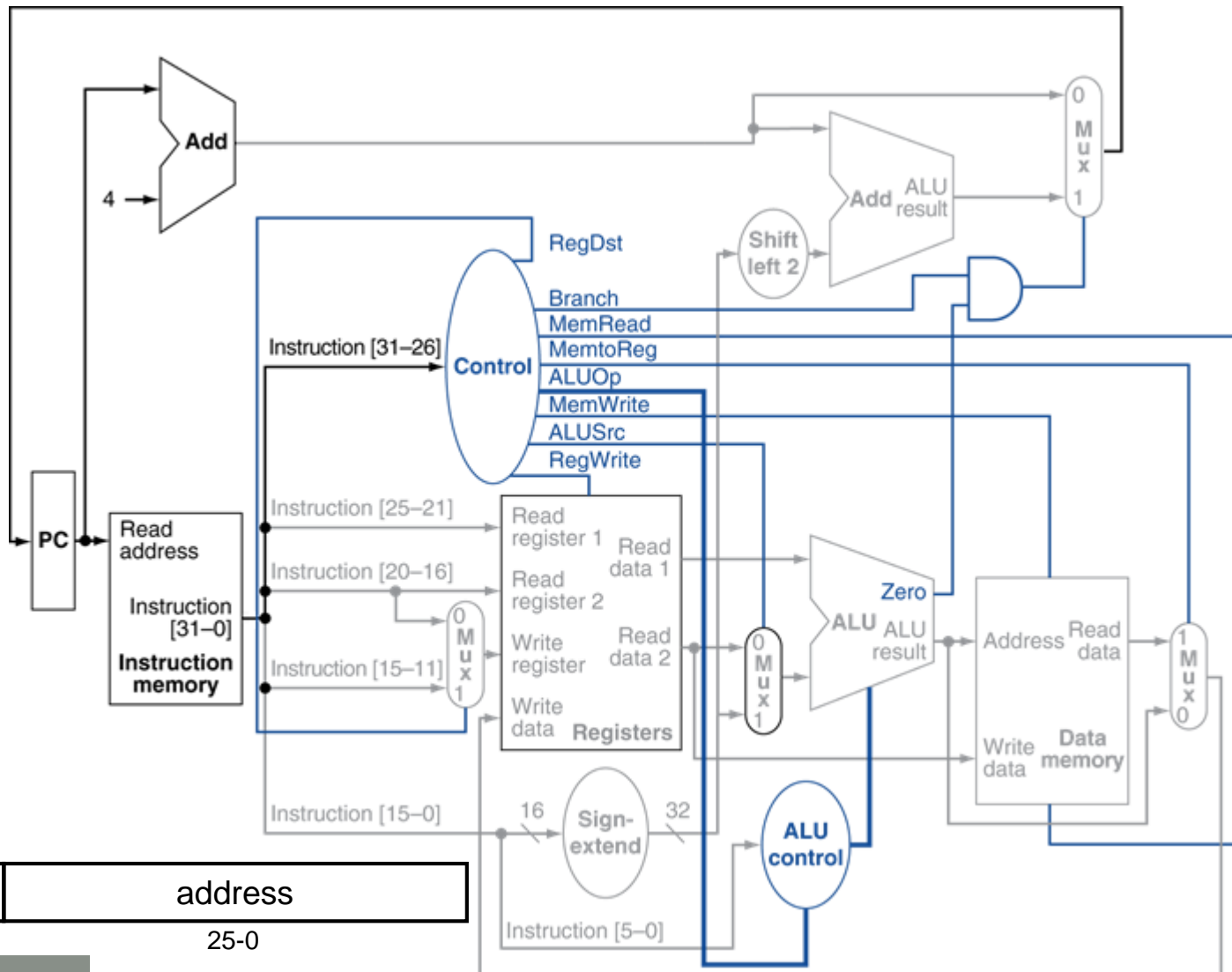

Jump address = PC+4 [31-28] : address × 4


Jump Instructions

Multiply
address
field by 4

 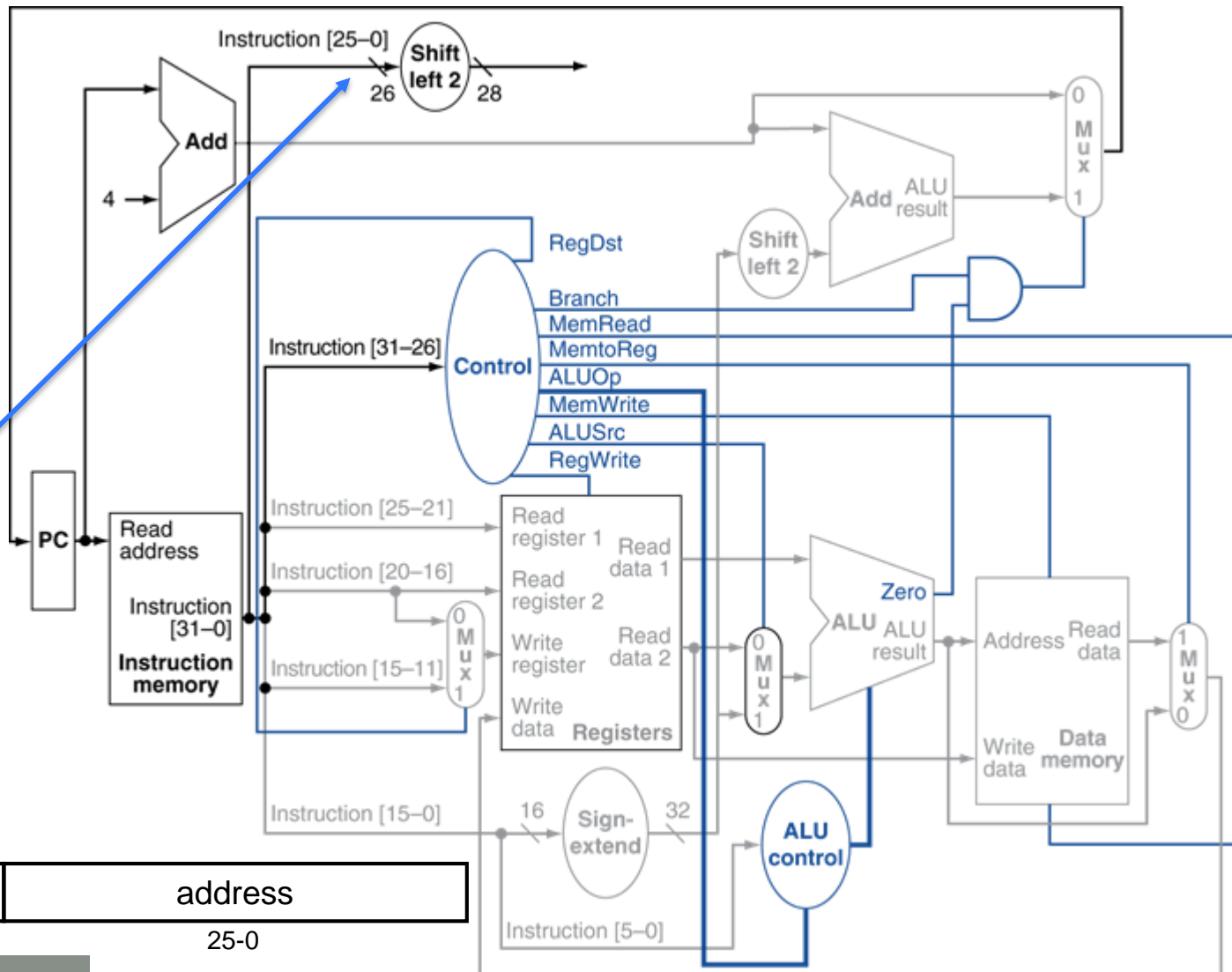


Jump address = PC+4 [31-28] : address x 4

Jump Instructions

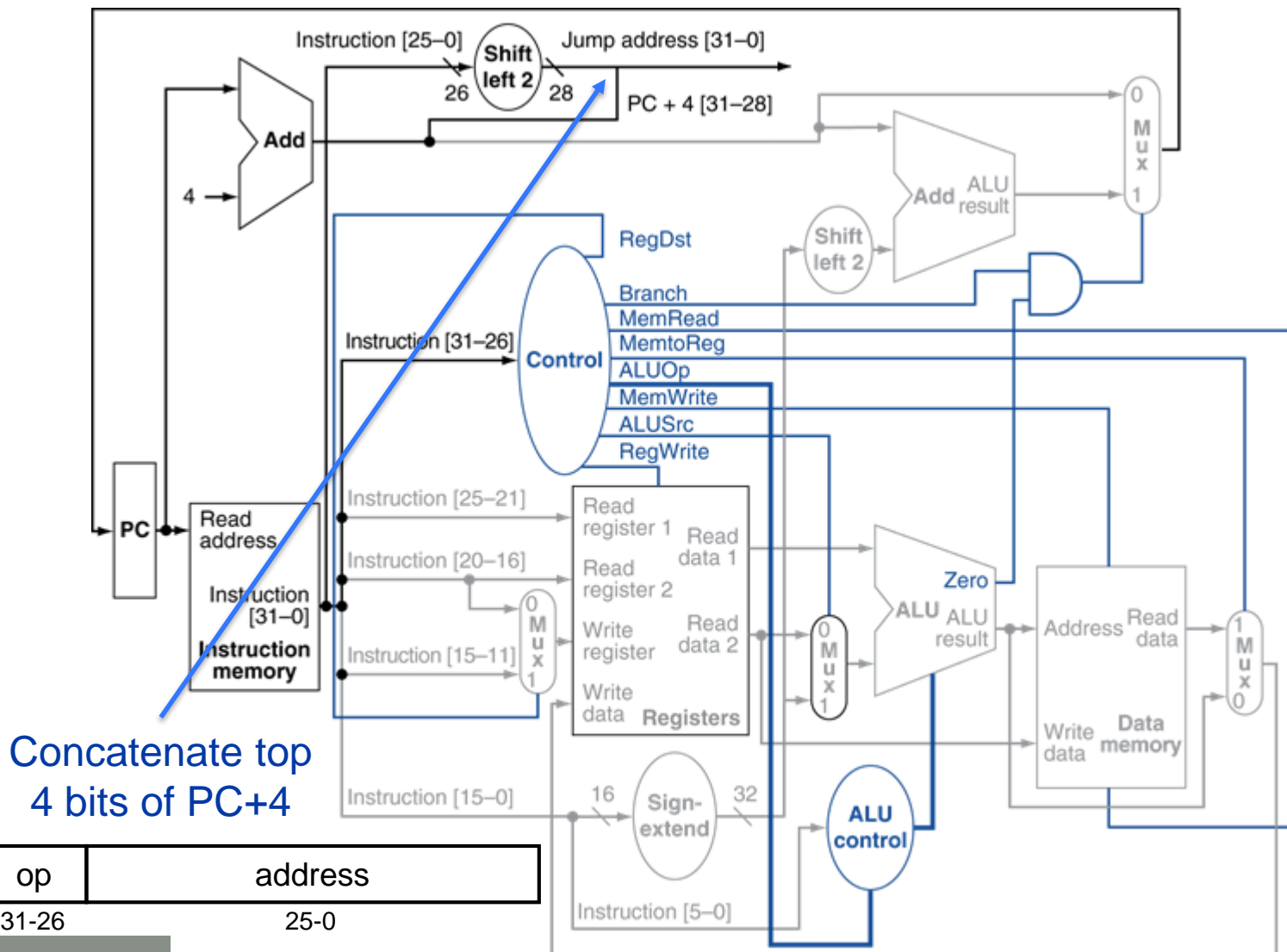


Jump address = PC+4 [31-28] : address x 4

Jump Instructions

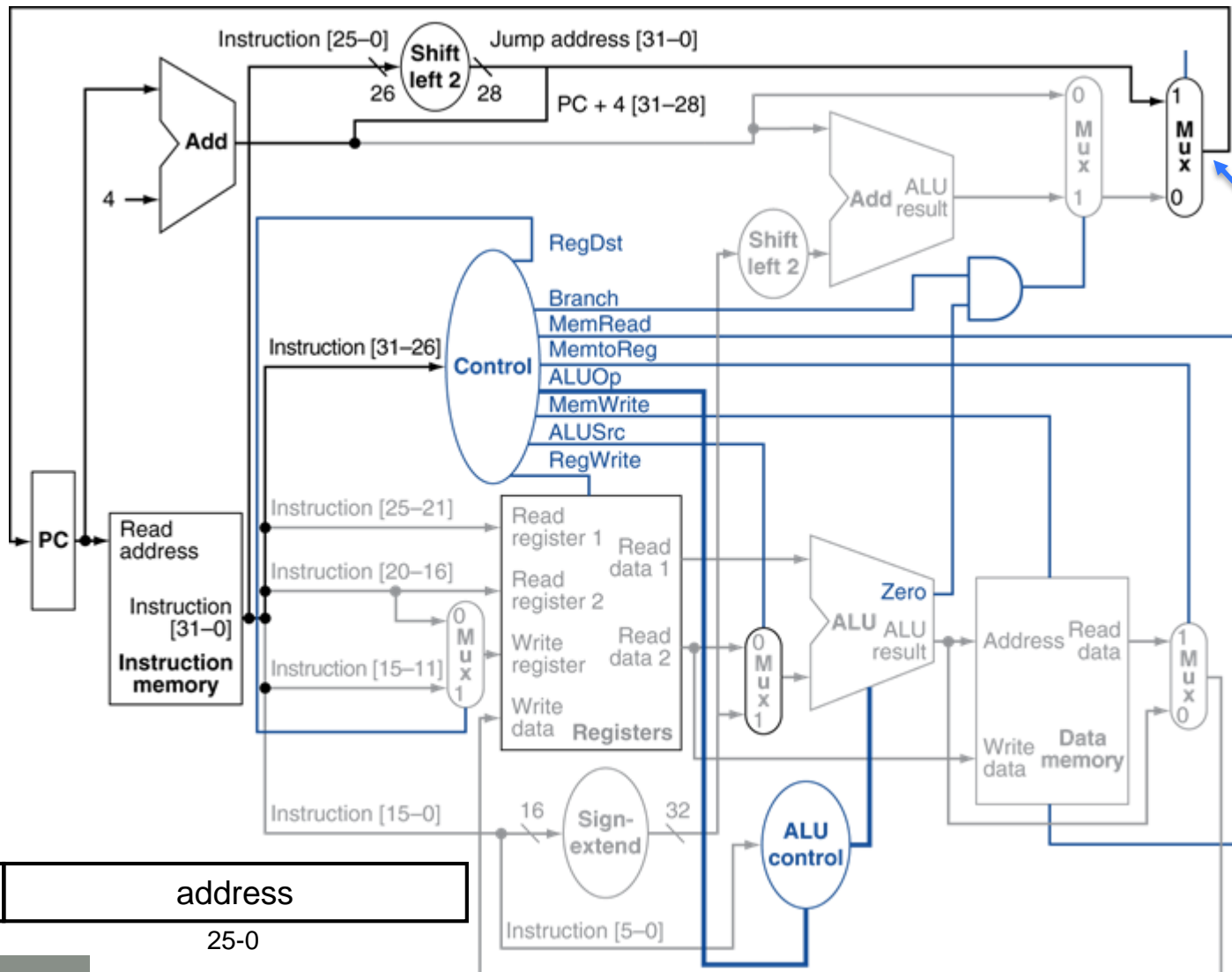


Use mux to select target address

 


Jump address = PC+4 [31-28] : address x 4

Jump Instructions

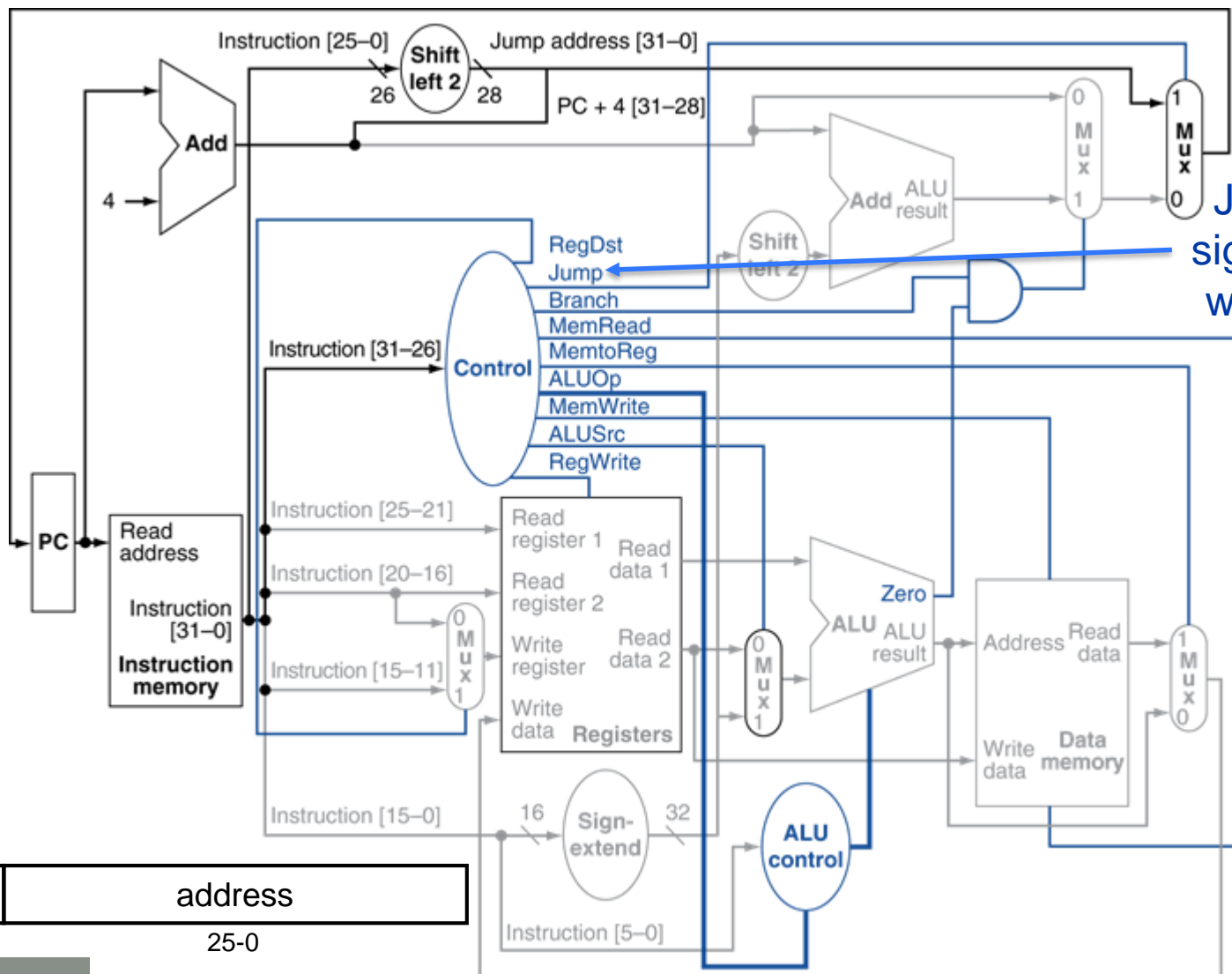


Jump control signal specifies what to select

Main Control Unit

 

| Instr[31-26] | RegDst | RegWrite | ALUSrc | ALUOp | MemRead | MemWrite | MemtoReg | Branch | Jump |
|--------------------|--------|----------|--------|--------------|---------|----------|----------|--------|------|
| R-type (000000) | 1 | 1 | 0 | func (10) | 0 | 0 | 0 | 0 | 0 |
| addi (001000) | 0 | 1 | 1 | add (00) | 0 | 0 | 0 | 0 | 0 |
| lw (100011) | 0 | 1 | 1 | add (00) | 1 | 0 | 1 | 0 | 0 |
| sw (101011) | d | 0 | 1 | add (00) | 0 | 1 | d | 0 | 0 |
| beq (000100) | d | 0 | 0 | sub (01) | 0 | 0 | d | 1 | 0 |
| j (000010) | d | 0 | d | d | 0 | 0 | d | d | 1 |

ALU Control Unit

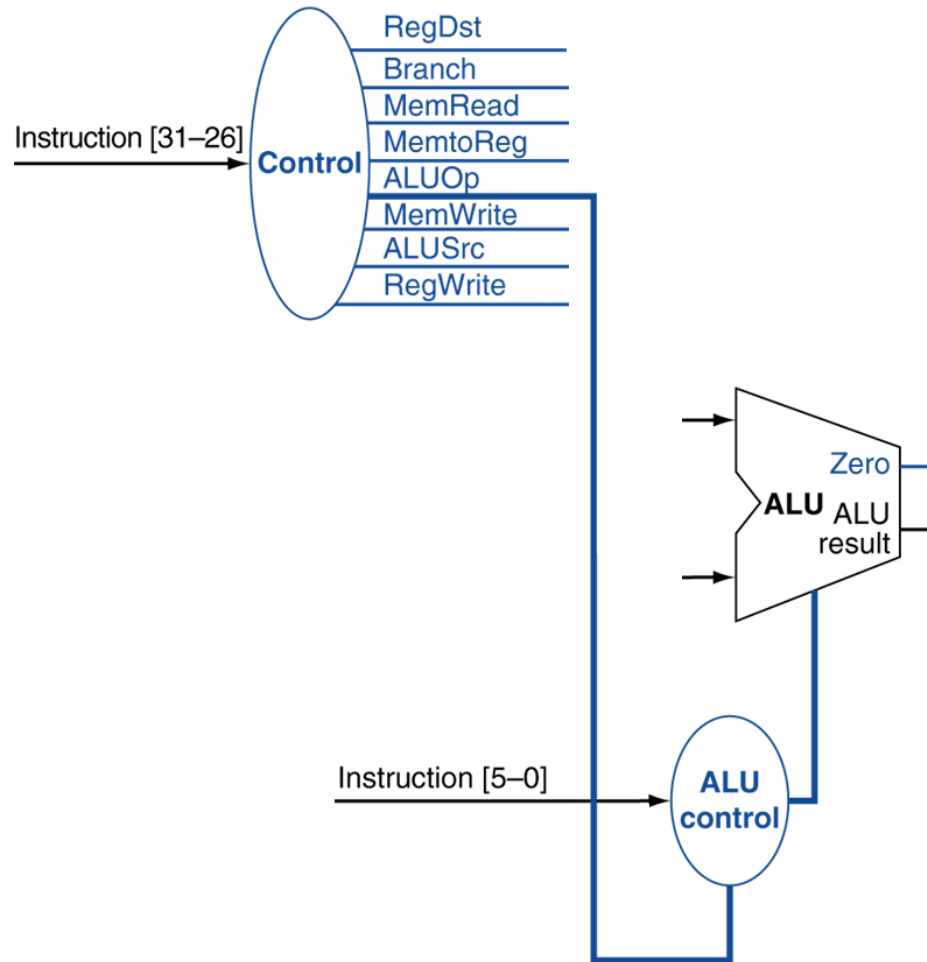

| ALUOp | Instr[5-0] | ALU Control Line |
|---------------|-----------------|------------------|
| funct (10) | add (100000) | add (0010) |
| | sub (100010) | sub (0110) |
| | slt (101010) | slt (0111) |
| add (00) | d | add (0010) |
| sub (01) | d | sub (0110) |

Textbook Sections

- The content in these slides corresponds to:
 - Textbook:
 - *Computer Organization and Design, 5th Edition by David Patterson and John Hennessy, Morgan Kaufmann, 2014.*
 - Sections:
 - 4.4